

amateur radio



SEE STORY ON PAGE 9



Registered at G.P.O., Melbourne, for
transmission by post as a periodical

Vol. 36, No. 9
SEPTEMBER
1968

30c

CITIZENS BAND CRYSTALS

To suit Japanese Walkie-Talkies and Transceivers. P.M.G. approved. Freq. 27.240 Mc. (Tx), 28.785 Mc. (Rx).

HCB/U Subminiature, 1/2 in. pin spacing, 27.240 or 28.785 Mc. \$3.50 each or \$6.50 a pair.

HC18/U Miniature 1/4 in. pin spacing, 27.240 or 28.785 Mc. \$3.50 each or \$6.50 a pair.

(HC18/U also available with flying leads)

Other Crystals available include 27.145 and 27.195 Mc.

Postage 10c.

MULTIMETER MODEL 200H

20,000 ohms per volt d.c., 10,000 ohms per volt a.c.

Specifications.—DC Volts: 0.5, 25, 50, 250, 500, 2,500. AC Volts: 0.10, 50, 100, 500, 1,000. DC Current: 0.50 uA.; 25, 250 mA. Resistance: 0.60K ohms, 0.6 meg. Capacity: 0.01-0.3 uF. (at AC 5v.); 0.0001-0.01 uF. (at AC 250v.). Decibel: Minus 20 db plus 22 db. Output range: 0.10, 50, 100, 500, 1,000. Battery used: UM3 1.5v., 1-piece. Dimensions: 3 1/4 x 4 1/2 x 1 1/2 in. Price \$11.00 Post Free. Complete with internal battery, testing leads, prods.

TURNTABLE BASES

Unpolished, to suit Garrard, Balfour, Princess, Dual 1010. Price \$7.00 each.

All channel Transistorised TV Antenna Boosters. Price \$10 each. Post 50c.

LATEST MINIATURE TYPE SILICON PLANAR N-P-N TRANSISTORS

Type 325—replaces BF115, SE1010

Type 327—replaces BC108, 2N3565, SE4002

Type 328—replaces BC109, SE4010

All 75c each, or three for \$2.00

Type 2N441 Transistor, \$2.40

KEW VACUUM TUBE VOLTMETER

MODEL K142

Specifications:

AC Voltage—Measurement Range, Sine Wave (in 7 ranges): 0.1-5v., 0.5v., 0.15v., 0.50v., 0.150v., 0.500v., 0.1500v.

Peak-to-peak (in 7 ranges): 0.4v., 0.14v., 0.40v., 0.140v., 0.400v., 0.1400v., 0.4000v.

Output (dBm): Minus 2 db to plus 65 db (in 7 ranges) (0 db equals 1 mw. in 600 ohm line): minus 20 to plus 5/16/25/36/45/58/65 dB.

Input Impedance: 1.4 megohms.

Input Capacitance: 30 pF or below (1.5/5/15/50/150v. range). 15 pF or below (500/1500 range).

Accuracy: Within plus or minus 5% full scale. Freq. Response: 30 c/s-50 Mc. within plus or minus 3%; 20 c/s-10 Mc. within plus or minus 10%.

DC Voltage—Measurement Range (in 7 ranges): 0.1-5v., 0.5v., 0.15v., 0.50v., 0.150v., 0.500v., 0.1500v.

Input Impedance: 1.4 megohms, 2 pF or below (using "D.C." Probe).

Accuracy: Within plus or minus 2% full scale.

Resistance—Measurement Range: 0.2 ohm-100M ohms (in 7 ranges): 0.1K, 10K, 100K, 1000K, 10M, 100M, 1000M ohms.

Accuracy: Within plus or minus 3% of the scale length.

Including D.C. Probe & Leads, Price \$52 inc. tax. R.F. and H.V. Probes extra.

30c Postage.

TRIO COM. RECEIVERS

Two Model 9R59DE, four bands covering 540 Kc. to 30 Mc., two mechanical filters for maximum selectivity. Product detector for SSB reception. Large tuning and bandspread dials for accurate tuning. Automatic noise limiter. Calibrated electrical bandspread. S meter and SFO. 2 microvolts sensitivity for 10 db. S/N ratio. Price \$175.

MULTIMETER, Model OL-64

20,000 ohms per volt d.c., 8,000 ohms per volt a.c.

Specifications:

DC Volts: 0-0.3, 1, 10, 50, 250, 500, 1,000, 5,000. AC Volts: 0-10, 50, 250, 1,000.

D.C. current: 0-30 uA.; 1, 50, 500 mA.; 10 A.

Resistance: 0-5, 500K ohms; 5, 50 megohms.

Decibels: Minus 20 to plus 22 db., plus 20 to plus 38 db.

Capacitance: 250 pF. to 0.02 uF.

Inductance: 0-5000 H.

Load current: 0-0.06, 0.6, 60 mA.

Self contained batteries: 22.5v. (BL-015) x 1, 1.5v. (UM3) x 2.

Size and weight: 6 x 4-1/2 x 2 in. 650 g.

Meter movement full sensitivity: 30 uA., F.S.D.

Price \$19.75, postage 25c.

F.M. TAXI RADIOS

T.C.A. (Phillips), Low Band, F.M. Mobile Units, 12 volt. Crystal locked, 120 kc. bandwidth. Operating frequency, approx. 80 Mc. Complete with all valves, vibrator and microphone. Suit Amateur conversion. Good condition.

OUR PRICE, LESS CRYSTALS, \$25.
Freight and Packing extra. Rail or IPEC.

TRANSISTOR INTERCOM UNITS

Four-Station: 1 master, 3 sub-stations. Three Transistors, 250 mW. Amplifier. Battery operated (Eveready 216), complete with battery, wire, staples and fitting instructions. Price \$19.75.

Two Station Model also available. Price \$10.50.

Three-Station intercoms, as per above, one master and two sub-stations. Price \$14.75.

FERROCART POCKET MULTIMETER

Model PT34. 300 uA. movement. AC and DC Voltages: 0-10, 50, 250, 500, 1,000v. Current ranges (mA.): 0.1, 100, 500. Ohms range: 0-100,000. Size 3 1/2 x 2 1/2 x 1 1/2 inches. Price \$2.75. Complete with leads.

BATTERY SAVER or A.C. ADAPTOR

A & R TYPE P664

- Unlimited operation of Battery operated Transistor Equipment from 240 volt A.C. Mains at negligible power cost.
- Ideal for 6 or 9v. Transistor Radios, Tape Recorders, Transistorised Small Amplifiers, and Test Equipment.
- Approved by Electric Supply Authorities.
- Maximum voltage limited to 7.75v. or 11v. at low current to protect transistors and capacitors.
- Filtered to ensure hum-free operation.
- 6 or 9v. (nominal voltage) selected by external switch.

Specifications.—Input: 220-240v. 50 c.p.s. Output: 6v. 7.75/11v. over no load to full load current range; or 5.6/7.75v. over no load to full load current range. Ripple voltage: 9v. output, 1.5 per cent. max. Ripple voltage: 9v. output, 0.5 per cent. max. Dimension 3 1/2 x 2 1/2 x 2 in. Price \$10.50.

WIRE WOUND POTENTIOMETERS

50 watts, 200 ohms. Price \$3.80.

No. 62 TRANSCEIVERS

Wireless Set No. 52 Mk. II. (Pye). Frequency range 1.6 to 10 Mcapies. In two bands. Built generator motor supply for 12 volt operation. Clean condition, \$30 inc. circuit diagram. Packing 75c F.O.R. Circuit diagram 95c extra.

BENDIX FREQUENCY METERS

BC221 Freq. Meters. Freq. range: 125 Kc. to 20 Mc. including crystals, A.C. power supply and calibration hook. As new, \$49.50. Packing 50c F.O.R. Also available (as above, BC221) but including modulation facilities, spare valves and headphones. Brand new in original packing case. Price \$65.

MO 65 METERS

New. Size: 3 1/4 inch, mounting hole 2 1/2 inch. All plus Postage 25c.

1 mA., 5 mA., 10 mA., 25 mA., 50 mA., 100 mA., 150 mA., 250 mA., 500 mA., ...	\$4.50
1 amp. D.C.	\$4.50
5 amp. D.C.	\$4.50
10 amp. D.C.	\$4.50
30-0-30 amp. D.C.	\$5.25
150 v. D.C., 30v. D.C., 300v. D.C.	\$5.00
300 volts A.C.	\$5.00

SOLDERING IRONS

Scope 6-second Standard	\$4.50
Scope De Luxe, Stainless Steel Barrel	\$3.00
Miniscopes	\$4.50
Birko 6-second	\$2.50
Transformer, suitable Scope or Birko	\$6.00
Resin Core Solder, 16 gauge, 40/60, 1 lb. pkt. \$1.20	
Resin Core Solder, 16 gauge, 60/40, 1 lb. pkt. \$2.20	

STEP-DOWN TRANSFORMERS

Primary: 240 volts. Secondary (switched): 24, 28 or 32 volts a.c. 30 cycle, 1.80 amp., with on/off switch and two outlet sockets. \$7.00, post \$1.00.

WIDE RANGE TWIN COLE LOUDSPEAKERS

5 in. Tweeter, 4,000-18,000 c/s, 15 watts r.m.s., 15 ohm V.C. \$4.50

8 in. Twin Cone, 40-12,000 c/s, 2, 8, 8, 16 ohms V.C., 8 watts r.m.s., 16 watts peak power handling \$7.50

Twin Cone, Elliptical, 85-10,000 c/s, 5 watts r.m.s., 15 ohm V.C., 7 watts peak power, 3.5 or 15 ohm V.C. impedance \$4.50

12 in. T.C., 45-10,000 c/s, 8 watts r.m.s., 10 watts peak, 2, 8 or 15 ohm V.C. impedance \$9.50

12 in. T.C., 30-14,000 c/s (in recommended enclosure), 8 or 16 ohm V.C., 20 watts r.m.s., 30 watts peak power \$41.50

S.W.R. METERS, MODEL KSW-10

Specifications.—Standing Wave Ratio: 1:1 to 10. Accuracies: Plus or minus 3 per cent. scale length. Impedance: 52 ohms and 75 ohms. Meter: 0-100 DC microamperes. Price \$19 inc. tax.

ALARM BELLS

(Parachute type), 6 volt. Suitable for Burglar Alarms, etc., complete with trip rope, etc. Price \$1.25, post 50c.

CALL BOOKS and LOG BOOKS

Price 75c each.



RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-4286 All Mail to be addressed to above address

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc.

"AMATEUR RADIO"

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA FOUNDED 1910

SEPTEMBER 1968

Vol. 36, No. 9

Editor:

K. E. PINCOTT VK3AFJ

Assistant Editor:

E. C. Manifold VK3EM

Publications Committee:

G. W. Baly (Secretary) VK3AOM
A. W. Chandler (Circulation) VK3LC
Ken Gillespie VK3GK
W. E. J. Roper VK3ARZ

Draftsmen:

Clem Allan VK3IV
Ian Smith 36 Green St., Noble Park

Advertising Enquiries:

C/o. P.O. Box 36, East Melbourne, Vic., 3002.
or
Mrs. BELLAIRS, Phone 41-3335, 478 Victoria
Parade, East Melbourne, Vic., 3002. Hours:
10 a.m. to 3 p.m. only.

Advertising copy should be forwarded direct
to the printers by first of each month.

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 478 Victoria Parade, East Mel-
bourne, Vic., 3002.

Printers:

"RICHMOND CHRONICLE," Phone 42-2419.
Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than
subscriptions, should be addressed to:

THE EDITOR,
"AMATEUR RADIO,"
P.O. BOX 36,
EAST MELBOURNE, VIC., 3002.

Acknowledgments will be sent following the
Committee meeting on the second Monday of
each month. All Sub-Editors should forward
their articles to reach "A.R." before the 5th
of each month. Any item received after the
Committee meeting will be held over until
the next month. Publication of any item is
dependent upon space availability, but in general
about two months may elapse before a
technical article is published after consideration
by the Publications Committee.



Members of the W.I.A. should refer all en-
quiries regarding delivery of "A.R." direct to their
Divisional Secretary and not to "A.R." direct.
Non-members of the W.I.A. should write to
the Victorian Division, C/o. P.O. Box 36, East
Melbourne. Two months' notice is required
before a change of mailing address can be
effected. Readers should note that any change
in the address of their transmitting station
must, by P.M.G. regulation, be notified to the
P.M.G. in the State of residence; in addition,
"A.R." should also be notified. A convenient
form is provided in the "Call Book".



Direct subscription rate is \$3.60 a year, post
paid, in advance. Issued monthly on first of
the month. February edition excepted.

CONTENTS

Technical Articles:—

	Page
A Simple Multipurpose Square Wave Generator	7
A Table Top S.S.B. Transceiver for Six Metres	4
A 40 Metre D.F. Rod with Transistor Pre-amplifier	6
Errata	10
Further Data on the Single Loop Triband Cubical Quad	8
Integrated Circuit I.F. Strip	8
Single Sideband Transceiver Development in Australia	9

General:—

Correspondence	15
DX	13
Federal Notes	16
Federal QSL Bureau	16
Field Day Fun—or—Heat, Files and Donga	12
New Call Signs	14
Prediction Charts for September 1968	11
W.I.A. D.X.C.C.	14
W.I.A. H.A.-VK-C.A. Award (S.w.I.)	14
Youth Radio Clubs Scheme of Australia	15

Contests:—

Contest Calendar	13
Join in the Victorian 160 Metre Contest	11

W.I.A. OFFICIAL BROADCASTS

NEW SOUTH WALES

VK2WI, Sundays, at 1100 hours E.A.S.T.
3595 Kc. a.m. 145.130 Mc. a.m.
7146 Kc. a.m. 146.000 Mc. f.m.
53.966 Mc. a.m. (53.950 Mc. f.m.
proposed shortly)

VICTORIA

VK3WI, Sundays, at 1030 hours E.A.S.T.
1625 Kc. a.m. 144.500 Mc. a.m.
3600 Kc. a.m. 145.254 Mc. f.m.
7146 Kc. a.m. 146.000 Mc. f.m.
53.032 Mc. a.m.

QUEENSLAND

VK4WI, Sundays, at 0900 hours E.A.S.T.
3590 Kc. 53.955 Mc.
7146 Kc. 144.1 Mc.
14.342 Mc.

SOUTH AUSTRALIA

VK5WI, Sundays, at 0900 hours C.A.S.T.
3.5, 14, 52 and 144 Mc. bands.

WESTERN AUSTRALIA

VK6WI, Sundays, at 0630 hours W.A.S.T.
3.655 Mc. a.s.b. 52.656 Mc. F3
7.080 Mc. a.m. 52.4 Mc. a.m.
14.100 Mc. s.s.b. 144.36 Mc. a.m.

TASMANIA

VK7WI, Sundays, at 1000 hours E.A.S.T.
3672 Kc., and re-transmitted by
representative stations on—
7146 Kc. 144.1 Mc.
53.032 Mc. 432.6 Mc.

BOOKS OF INTEREST FOR AMATEUR OPERATORS

- ★ A.R.R.L. — **THE RADIO AMATEUR'S HANDBOOK** — 45th Ed., 1968 Edition **Price \$6.10 Posted**
The standard reference work and text for everyone—Hams, Experimenters, Students, Engineers, Laboratory Men, Technicians.
- ★ ORR — **THE RADIO HANDBOOK** — 17th Edition **Price \$13.45 Posted**
Tells how to design, build and operate the latest types of Amateur Transmitters, Receivers, Transceivers and Amplifiers.
- ★ STONER & EARNSHAW — **THE RADIO TRANSISTOR HANDBOOK** **Price \$6.65 Posted**
This up-to-date Handbook covers a wide range of communication for both Amateur Radio and Commercial Applications.
- ★ A.R.R.L. — **THE RADIO AMATEUR'S V.H.F. MANUAL** **Price \$3.73 Posted**
- ★ A.R.R.L. — **UNDERSTANDING AMATEUR RADIO** **Price \$3.00 Posted**
- ★ A.R.R.L. — **THE A.R.R.L. ANTENNA BOOK** **Price \$3.00 Posted**
- ★ A.R.R.L. — **SINGLE SIDEBAND FOR THE RADIO AMATEUR** **Price \$3.73 Posted**
- ★ A.R.R.L. — **THE MOBILE MANUAL FOR RADIO AMATEURS** **Price \$3.73 Posted**
- ★ A.R.R.L. — **THE RADIO AMATEUR'S LICENSE MANUAL** **Price 85c Posted**

McGILL'S AUTHORISED NEWSAGENCY

Established 1860

The G.P.O. is opposite

183-185 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones 60-1475-6-7

FOSTER DYNAMIC MICROPHONES

SPECIFICATIONS:

Output Impedance 50 ohms or 50K ohms
Effective output level —55 db. [0 db. — (one) 1V. Microbar]
Frequency response 50 to 15,000 c.p.s.


OMNI-DIRECTIONAL DYNAMIC:

Plastic Diaphragm. Swivel fits $\frac{5}{8}$ " 26 t.p.i. Stands
Size: 4½" long, 1¼" diameter. Colour: TWO-TONE GREY.
Cable: 12 ft. of P.V.C.

Retail Price 50K ohms: **\$9.60** + Sales Tax \$1

Retail Price 50 ohms: **\$9.40** + Sales Tax 98c

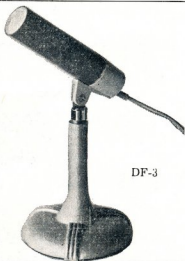A QUALITY PRODUCT FOR TAPE RECORDERS & P.A. USERS



DF-3



Marketed by **ZEPHYR PRODUCTS PTY. LTD.**


70 BATESFORD ROAD, CHADSTONE, VIC., 3148

Phone 56-7231

Manufacturers of Radio and Electrical Equipment and Components

W.A.— Agents: D. K. Northover & Co.; S.A.— Neil Muller Ltd.; Tas.— Homecrafts (Tas.) P/L; N.S.W.— Jacoby, Mitchell & Co. P/L; Old.— T. H. Martin P/L

Modern SSB by Yaesu!

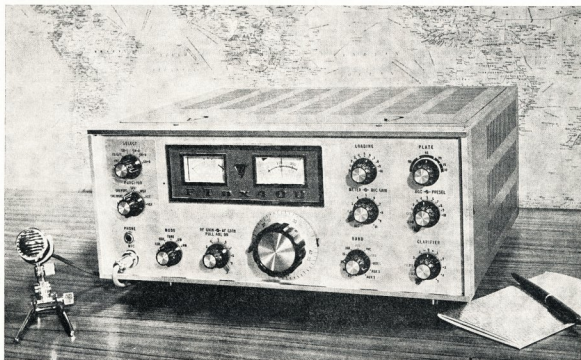

NEW MODEL TRANSCEIVER - FTDX-400

— THE "EXTRAS" ARE STANDARD EQUIPMENT —

COMPARE THE FEATURES:

- ★ Five bands, including full coverage on 10 metres.
- ★ A powerful 400 watts (500 watts speech peak SSB input).
- ★ Power Supply built in, 230v, 50 cycles AC (no extra charge!).
- ★ Selectable USB/LSB, CW and AM, normal or break-in keying.
- ★ Carrier input adjustable for safe tune up.
- ★ PA uses pair of new heavy duty pentodes, type 6KD6, 33 watt plate dissipation.
- ★ VOX is included, as well as PTT and panel control.
- ★ 100 kc. and 25 kc. dual calibrator.
- ★ Sidetone CW monitor.
- ★ Multi-scale panel meter, fully calibrated, provides direct reading of PA current, plus relative power output, ALC indication, Rx "S" units.
- ★ Offset tuning, plus or minus 5 kc. is provided by clarifier control, which is selectable Off, Rx, and Tx.
- ★ VFO dial readout of 1 kc.
- ★ Dial forward reading all bands.
- ★ Provision for external VFO for split frequency operation, plus built-in four crystal locked channel facility.
- ★ Adjustable VFO tuning knob tension.
- ★ Fast and slow selectable receiver AGC.
- ★ All plugs, circuit and instruction manual provided.
- ★ PTT microphone included—free.
- ★ Superbly neat construction, very accessible for servicing.
- ★ Solid, charcoal blue cabinet with lift-off lid, 15¼ x 6¼ x 13¾ inches. Matt finish aluminium panel.
- ★ 18 valves, 9 transistors and 33 diodes.

Our policy: 90-day manufacturer-backed warranty. All sets tested before despatch. After-sales service and spares availability.

FOR PRESTIGE PERFORMANCE — CHOOSE YAESU

Write for illustrated leaflets.

Australian Agents:

BAIL ELECTRONIC SERVICES

60 Shannon St., Box Hill North, Vic., 3129. Phone 89-2213

Rep. in N.S.W.:

MOSMAN RADIO SERVICES

P.O. Box 198, Tamworth, N.S.W., 2340

A Table Top S.S.B. Transceiver for Six Metres

A. S. LUNDY,* VK2ASI

HAVING built a much transistorised copy of the Swan 240 for use as a mobile rig and found it an ideal layout to "home brew," it was decided to try a 6 metre version along the same lines. As the unit would be used almost exclusively for working sporadic E openings, high power and performance was not really necessary, hence the use of a 2E26 final and a valve receiver front end. The performance nevertheless is quite adequate, with at least 30 watts p.e.p. output and a receiver that will hear 0.2 microvolt above the noise. The output level is ideal for driving an "afterburner" and a FET pre-amplifier would no doubt improve the receiver to match.

CHASSIS CONSTRUCTION

The chassis was formed from 16g. half hard aluminium sheet (Fig. 1). Pop rivets were used wherever possible and self tapping screws elsewhere. Some form of chassis bender is needed, if only a large vice and some pieces of angle iron. All bends are made in the same direction. A matt finish can

cover has a similar pattern at $\frac{1}{2}$ " centres over the p.a. box. There is also a gap of $\frac{1}{4}$ " between the top of the front panel and the underside of the top cover, also for ventilation purposes.

RECEIVER CIRCUIT

The receiver front end consists of a pair of 6AK5s as r.f. stage and mixer. Output from the mixer is coupled through IFT3 into the 6.4 Mc. crystal filter. The 250 pF. and 470 pF. capacitive dividers provide low impedance into the filter. The filter was constructed from FT243 surplus crystals using the sweep unit described in December 1967 "A.R.", page 10. The filter crystals are mounted on a piece of matrix board, three holes wide by seven holes long, and the whole unit then supported on two $\frac{1}{4}$ " bolts.

6.4 Mc. was the highest frequency that a quantity of surplus crystals were available in and this, combined with the fact of no harmonics in the 6 metre band and a reasonable conversion ratio to 6 metres, led to the choice of this frequency. The author can supply a

incoming 52.0 to 52.5 Mc. signals, produces the 6.4 Mc. i.f. frequency.

Crystals on 34.5 Mc. and 36.0 Mc. can also be switched in so as to give a tuning range from 51.5 to 53.5 Mc. in segments of 500 Kc. This arrangement gives a constant tuning rate per segment and adequate stability.

Output from the v.f.o. mixer is passed through three tuned circuits to the grid of the 12BA6 v.f.o. amplifier. The four tuned circuits (L16, L17, L18 and L19) are adjusted so as to provide a bandpass between 45 Mc. and 47 Mc. This adjustment is easily done by disabling the v.f.o. oscillator by removing the 33 pF. coupling capacitor to the tuned circuit, coupling a signal generator to the base of the emitter follower with a 100 pF. capacitor, and detecting output in the 12BA6 v.f.o. amplifier plate circuit by means of a 2-turn link, a OA91 diode and a 50 or 100 micro-ampere meter.

Remove the overtone crystals so as to disable the overtone oscillator, then slowly tune the signal generator across the 45-47 Mc. range. Adjust the four tuned circuits to get a suitable bandpass, which should come out with quite steep sides and only a 3 db. hole in the middle. It is surprising just how effective this simple arrangement is.

The complete v.f.o., overtone oscillator and mixer are mounted on matrix board, 7 holes wide and 5 inches long. L17 and L18 mount on a small additional piece attached to the front side with Araldite.

The v.f.o. coils, L13 and L14, are mounted in the v.f.o. box alongside the tuning capacitor.

The former for L13 is a threaded bakelite one from the crystal oscillator section in the SCR522 units. The variable inductance, L14, is used for band-setting and is wound on a 7 mm. slug tuned former with $\frac{1}{2}$ " square base. The same formers are used in the three i.f. transformers also, and are available from the W.I.A. N.S.W. Division, as are the 0.5-60 pF. v.h.t. trimmers used throughout the transceiver, and the 25 pF. polar tuning capacitors.

As crystal locked transmitters seem to still be in the majority on 6 metres, it was necessary to include a function which allowed one to call CQ, then tune the band, so a crystal oscillator was incorporated which could, if desired, be used to lock the transmit frequency, while the v.f.o. was used to tune the receiver. This function is controlled by a front panel switch SW2 and relay No. 2.

When the switch is on "transceive" position, operation is on the one frequency. When on "crystal" position the transmitter is crystal locked while one tunes the receiver with the v.f.o. The frequency of the crystal lies between 10.6 Mc. and 11.1 Mc., the same as the v.f.o. it replaces. It would be possible to use an overtone crystal between 45.6 Mc. and 47.1 Mc. instead

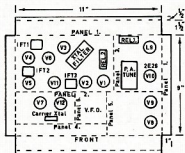


FIG. 1. CHASSIS LAYOUT.

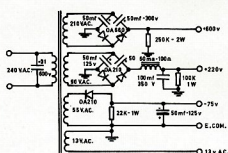


FIG. 3. POWER SUPPLY

be obtained on the chassis by etching in 5% sodium hydroxide for about 5 minutes. This also removes most of the marks and scratches that invariably appear after the cutting and bending work. Ventilation holes are drilled around each valve socket, 6 holes round the 7-pin and 8 holes around the 9-pin with a double row around the 2E26 socket.

The tuning drive mechanism is a copy of the Swan 350 arrangement and consists of two 6 to 1 Jackson verniers, 1 brass spacer and the spun aluminium course tuning knob and the outer bakelite fine tuning knob. This assembly is available from Ham Radio Suppliers of Melbourne. The first vernier is attached to the v.f.o. box wall and the second vernier to the front panel with the brass spacer between it and the panel.

The bottom cover has a pattern of 3/16" holes drilled in it at 1" centres to provide ventilation, while the top


limited number of filter units, aligned and mounted at \$7 each for those who do not wish to construct their own.

Output from the filter goes to the 1st i.f. amp., then is capacitively coupled out of IFT1 to the second i.f. stage. The cathodes of these two stages and the 6AK5 r.f. stage are tied together through the r.f. gain control. A.g.c. is applied to the r.f. stage and second i.f. stage. One half of a 12AT7 is the product detector, the other half serves as the first audio. A pair of OA91 diodes as a voltage doubler provide the audio-derived a.g.c. voltage. The audio output is provided by a 12AQ5 which is only coasting along but still provides all the audio required.

HETERODYNE V.F.O.

The v.f.o. runs at 10.6 to 11.1 Mc. and after passing through an emitter follower isolation stage is mixed with 35 Mc. energy from an overtone crystal oscillator to give an output of 45.6 to 46.1 Mc. which, when mixed with the

*36 Ocho Street, Inverell, N.S.W., 2360.

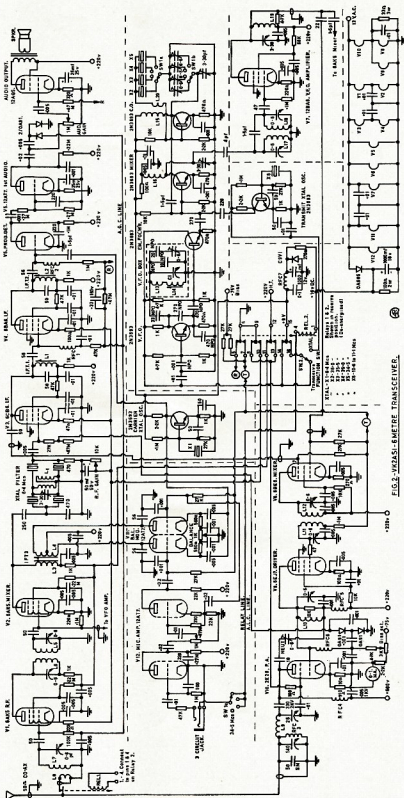

of the whole v.f.o. assembly, but the use of the lower crystal has some advantages, namely:

- (1) A cheaper crystal.
- (2) An overtone crystal would require a tuned circuit and feedback link.
- (3) Three crystal locked positions are available from one crystal, i.e. if one used a crystal on 10.7 Mc. then one could operate on 52.1, 52.8 or 53.1 Mc., depending on which 500 Kc. segment was selected.

Inadvertent transmitter operation in the 51.5 to 52.0 Mc. range is avoided by means of switch IC which disables the push to talk circuit when this segment is selected.

The 0.5 to 6 pF. trimmer and the 20 pF. N750 capacitor provide negative temperature co-efficient to enable drift in the v.f.o., due to temperature rise, to be compensated for. The prototype unit required the full amount and now has less "driftitis" than a lot of the crystal locked transmitters on this band.

Front panel controls are from the left: 1, audio gain; 2, r.f. gain; 3, band selector Sw.1; 4, microphone socket; 5, microphone gain; 6, balanced modulator control; 7, p.a. bias; 8, crystal-transceiver function switch. The p.a. tune and load controls are alongside the cathode current meter, which is a MR2P type. The black pointer knobs are available from the W.I.A. NSW. Division Equipment Store.

All components were mounted on miniature tag strips around the relative valve sockets, the coils were also mounted in this manner, while the 0.5-6 pF. v.h.f. trimmers were mounted through 1" holes with a self tapping screw so that they could be adjusted from the top side of the chassis.

The v.f.o. tuning capacitor is a Polar single gang type C18-02 of 25 pF. Plates are removed from it so that only four stator and four rotor plates are left.

TRANSMITTER

Audio from a high impedance microphone goes to one half of a 12AT7, then to the other half which is a phase-splitter and provides push-pull audio to the grids of a second 12AT7 which serves as a balanced modulator. Originally a 7360 beam deflector valve was contemplated here but as they are \$5 and VK2ASI has plenty of five for \$2 12AT7s around, the latter were tried and found to be completely satisfactory. R.f. in parallel from the carrier crystal oscillator is applied to the 12AT7 cathodes and balance achieved by means of a variable cathode resistor.

The double sideband output is coupled into the crystal filter through 1FT3 and is amplified by the 6CB6 first i.f. stage. The second i.f. stage, product detector and audio output stages are disabled by the application of -75 volts to their control grids. S.s.b. output from the first i.f. stage goes to the injection grid of the 6BE6 mixer, while output from the heterodyne v.f.o. goes to the control grid.

Some doubt was entertained as to the effectiveness of a 6BE6 at 52 Mc., so

FIG. 2—VZAS1—6-METRE TRANSCEIVER.

a 6AG5 was tried instead at one stage, but was soon changed back to the 6BE6.

Inductive coupling between L11 and L12 transfers the energy to a 6EJ7, which does an adequate job as a driver and does not need to be neutralised, although the small value resistor in the grid circuit is a necessary item.

The signal is then capacitively coupled into the 2E26 grid, which should have approximately -30 volts bias on it, to produce a standing current of 10 mA. on the cathode current meter with the plate and screen voltages shown. Output is into a pi-coupler, the tuning capacitor is the same type as used in the v.f.o., and the 140 pF. load capacitor is from a BC811 WW2 walkie-talkie. Another 25 pF. capacitor could be used here with 150 pF. or so of fixed mica capacitor, instead of the BC611 unit.

Cathode current kicks up to 10 mA. to 40-50 mA. with speech and a steady whistle should give 70-80 mA. cathode current and about 15 watts into a wattmeter. Plate efficiency is then close to 50%. A fraction of a milliamp. of grid current may also be drawn under these conditions.

A.L.C. is provided by means of a pair of OA91 diodes as a voltage doubler and applied to the 6CB6 first i.f. stage. Neutralisation of the 2E26 is provided for, although the author has found that very little, if any, was needed. The main requirement being that the final is heavily loaded. A lightly loaded final cannot be successfully tamed (not mine anyway). The loading and tuning is always adjusted, with the aid of a s.w.r. meter, so that one is getting maximum r.f. output.

COILS AND SPECIAL COMPONENTS

L1 and L2: 40 turns of 28 B. & S. enamelled copper wire on a 7 mm. slug tuned former. L3: 20 turns as above. L4: 2 by 20 turns bifilar wound 33 B. & S. spaced $\frac{1}{8}$ " from L3. The formers used for the above coils are $\frac{1}{2}$ " long with a $\frac{1}{4}$ " base and are enclosed in a can. Available from the W.I.A. N.S.W. Div.

The following coils are all close-wound with 20 B. & S. enamelled wire and are $\frac{1}{2}$ " inside diameter. L5: 12 turns, L6 12t., L7 12t., L8 2t., L10 6t., L11 9t., L12 8t., L15 12t., L16 10t., L17 14t., L18 9t., L19 7t., L20 2t.

P.a. coil L9 is 5 turns of 10g. copper wire or $\frac{1}{4}$ " copper tubing with $\frac{1}{8}$ " spacing between turns and a $\frac{1}{4}$ " leg at each end. $\frac{1}{2}$ " inside diameter.

L13 is the coil and threaded former from the SCR322 crystal oscillator and is 9 turns spaced one turn on $\frac{3}{8}$ " diameter. The winding was given a coat of Araldite.

L14 is 8 turns of 20 B. & S. on a 7 mm. slug tuned former. It is also given a coat of Araldite. Make sure the slug is being firmly held in place with rubber strip as a loose slug here will really ruin the v.f.o.'s mechanical stability.

RFC1, 2, 5, 6 and 7 are 560 uH. video peaking chokes available from Ham Radio Suppliers. RFC3 and 4 are 24 B. & S. close wound on a $\frac{1}{4}$ " former, $\frac{1}{2}$ " long.

Relay 1 is a small single change-over type, ex disposals.

Relay 2 is a miniature plug-in type available from S.T.C. at a reasonable price. Its type number is 250AKO.

The power supply transformer was rewound from a discarded one that had a shorted-turns secondary. All windings except the primary were removed and new secondaries were wound

on at 3 turns per volt. The use of voltage doubling circuits reduced the amount of rewinding necessary. The power supply was constructed on a $\frac{5}{8}$ " x 7" chassis of the same design as the transceiver.

Switch 1 is a miniature 3-pole, 4-position M.S.P. type 73625 A1.

Switch 2 is a miniature 6-pole, 2-position M.S.P. type 73652 A1.

A 40 Metre D.F. Rod with Transistor Pre-amplifier

The direction finding rod to be described here was built as an easy way into hidden transmitter hunts at conventions. The direction finding abilities of the rod are quite good, but its signal pick-up is virtually nil compared with the mobile whip. To help overcome this, a single stage transistor r.f. amplifier was added as an outboard unit and this improved the performance remarkably.

Signals that were inaudible without the pre-amplifier became S5 to S6 with the pre-amplifier. It would appear that the 30 db. plus gain of the SE1001 is being obtained, while the increase in background noise is just noticeable.

The d.f. rod is built from a piece of $\frac{1}{2}$ " inch ferrite rod at least 6 inches long, mounted on a U shaped piece of perspex with a handle underneath. The winding is "dipped" to frequency with a g.d.o. coupled with a 2-turn link to the co-ax. lead.

The pre-amplifier is constructed on a piece of matrix board 2 inches square. A shield runs across the centre of the board. Coils L3, L4 and L5 are wound on 7 mm. slug tuned formers with $\frac{1}{2}$ " inch square bases, obtained from the VK2 Division Store. The SE1001 draws approximately 2 mA. and a small 9 volt battery is used as the supply.

L5 and the 0-12 pF. v.h.f. trimmer provide for neutralisation of the SE1001 which is necessary. With the trimmer at minimum, the SE1001 will probably oscillate, this being obvious by the infinite number of whistles and squeaks

in the 40 metre receiver. Start winding the trimmer in and the oscillation should stop, although the background "hiss" will be high, but will decrease until a point of least noise is reached at about 6 pF. Further capacitance will cause an increase in the noise till the stage oscillates again at full capacitance. The setting that gives the least noise is the correct point. This adjustment is done with the d.f. rod connected to the pre-amplifier and L3 and L4 set near frequency with the g.d.o. Now peak L3 and L4 on a signal near 7050 Kc. and finally re-touch the neutralising capacitor.

The rod is hand-held by means of the short handle, and satisfactory results are obtained even with the rod held just outside the car window. The signal nulls off the ends of the rod are quite sharp and can be missed if the rod is turned too rapidly. Being hand-held, it is easy to sight along the rod and get a visual heading from it.

No difficulty has been experienced in determining whether the signal is coming from "that a way" or from 180 degrees back the other way, as this can be determined by taking a second heading about a quarter of a mile away from and at right angles to the first one so as to get a cross reference. In some cases a knowledge of the area will eliminate one direction due to the terrain or available access. A sensing whip can be added if desired, but may be more of a physical hindrance than anything else.

—A. S. Lundy, VK2ASI

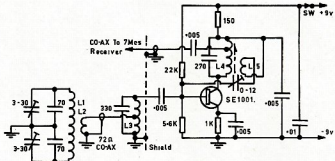


FIG. 1. FORTY METRE D.F. ROD & PRE-AMPLIFIER. (R)

COIL DATA

L1-14 turns on $\frac{1}{2}$ " inch ferrite rod spread over 5 inches, 20 B. & S.
L2-4 turns over centre of L1.

L3-15 turns tapped 5 turns from earth end, 20 B. & S. on 7 mm. slug tuned former.
L4-20 turns tapped 4 turns from "cold" end. 20 B. & S. on 7 mm. former.
L5-7 turns of 28 B. & S. wound over L4.

A SIMPLE MULTIPURPOSE SQUARE WAVE GENERATOR

JIM JONES,* VK2ZET (Ex VK3ZEW)

ON building an oscilloscope and associated probes, I discovered I would require a square wave generator to help me align my low capacitance attenuator probe.

The oscilloscope only incorporated one internal calibration voltage, as this was only a one volt peak to peak 50 cycle sine wave, it was quite useless for the purpose I required.

As the probe had a small variable frequency compensation capacitor (which had to be adjusted), it was nearly essential to use a waveform that would give a wide range of frequencies in one signal—so a square wave was chosen.

The capacitor had to be adjusted so that it gave an equal attenuation over the required spectrum of frequencies (for which the probe was intended).

So once again, I dug deep into my little junk box and dug out several transistors, a couple of resistors and capacitors plus several diodes.

After surveying my components I decided the frequency of the unit was relatively unimportant except the output was to be as square as possible (with a relatively short rise time).

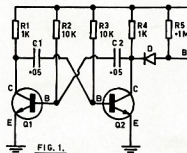


FIG. 1.

All resistors 1/2 watt, 10% tolerance.
All capacitors 20 volt working.
Diodes: Three 1N759 or any silicon signal diodes.

CIRCUIT DESCRIPTION

The simplest circuit I could think of at the time with a square wave output was an astable multivibrator.

The output of this circuit, as shown by the waveform diagram, was relatively poor although it was ample to trigger the next stage which was an emitter follower.

The emitter follower served two purposes: (1) isolation between the multivibrator and the output, and (2) it gave a power gain to the signal, although the voltage gain of the stage was less than unity.

The output was coupled from the emitter follower through an integrating circuit to the limiting circuit.

The limiter basically consists of two silicon diodes placed in the opposite direction.

The output was now both square and a constant 1.2 volts peak to peak. After


running the system for several hours and monitoring the output, it was found to be quite ample for my requirements.

The circuit is basically an astable multivibrator whose frequency depends on the time constant of the capacitors and resistors used in the base and collector circuit. This circuit will work with nearly any type of small signal audio or switching transistors. I checked the circuit with both PNP and NPN transistors, the only change necessary was to reverse the leads on the battery.

THEORY OF OPERATION

Due to variation in the components, one transistor conducts before, or a little more heavily, than the other.

In our case let us assume that transistor Q2 is conducting more than Q1, more current flows in the base circuit of Q2, resulting in a rapidly increasing collector current. The increasing voltage at the collector of Q2 is coupled through C2 to the base of Q1, decreasing the base and collector current in Q1. The collector voltage on Q1 suddenly becomes more positive, coupling a positive voltage to the base of Q2. This action drives Q2 into saturation and

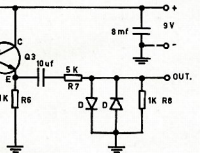

Transistors: Three 2N2102 NPN, or any audio or switching; or three 2N404 PNP or any audio or switching, but reverse battery connections.

Q1 into cut-off. The action happens so quickly that capacitor C2 does not discharge, and the entire voltage increase of the collector of Q2 appears across R4 and at the base of Q1. Capacitor C2 then discharges until Q1 conducts, and the cycle is completed. The resulting output from the collector of Q1 is a square wave whose amplitude is dependent on the supply voltage.

The output of the multivibrator is taken off the collector of Q2 and is coupled to the next stage via diode D1. This diode conducts when Q2 is conducting a saturation, also when this diode is conducting Q3 is cut off; secondly, when the diode is off Q3 will conduct and an output will be present.

The output from this stage is taken across the emitter resistor. It is then coupled through an integrating circuit which does not allow the d.c. level to pass (the output swings equal around a zero axis).

The limiter is basically two silicon diodes placed in the opposite direction, each diode will conduct when its forward biasing point is reached. This, in silicon diodes, is approximately 0.6 of a volt, hence the output is now a square wave with a maximum swing of 1.2 volts peak to peak. If germanium diodes were used the output would only be 0.4 volt peak to peak.

WAVE FORMS.

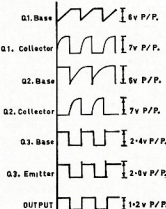


FIG. 2.

Waveforms taken with following settings: 1 volt/cm, plus internal sync. All waveforms are shown but as the c.r.o. had only an a.c. input, no reference to the d.c. was able to be shown.

The following waveforms are typical of those which will be obtained when testing an amplifier:—

- (A) Output of generator.
- (B) Following are outputs of amp. with differing faults:
- (C) No defects.
- (D) Loss of low frequency gain with leading low frequency phase shift.
- (E) Excessive low frequency gain with lagging low frequency phase shift.
- (F) Poor middle and high frequency response.
- (G) Excessive high frequency response and ringing.

CONCLUSION

This circuit thus enabled me to set up my oscilloscope probes and the actual oscilloscope. I have also used this circuit for checking audio amplifiers and as a source for a Morse practice system. It can also be used for many other purposes such as signal injection for fault finding, both r.f. and a.f. circuits.

* 1 White Street, Durlington Point, N.S.W., 2706.

Further Data on the Single Loop Triband Cubical Quad

The original article appeared in "A.R." of April 1968, and the author has forwarded more details of these quad elements as a supplement for those interested in such antennas. Tuning seems far less critical compared with a Yagi beam using this system because the quad element has more wire (length).

DATA FOR FIGURE 1

- L1—7 turns, 37 mm. diam., 16 mm. long.
L2—4 turns, 37 mm. diam., 18 mm. long.
L3—4 turns, 37 mm. diam., 9 mm. long.

1 mm. copper wire was used for the coils.

Aerial Resonances S.W.R.

14.15 Mc.	~1:1
21.3 Mc.	1:1.3
28.6 Mc.	1:1.5

Select reflector and director frequencies as usual. Spacing for 21.3 Mc.

Capacitors: Ceramic 38 mm. diam., or pieces of co-ax. cable, 10 kva., NPO.

Fine tuning:

- 14 Mc.: Wire length or L1.
21 Mc.: C1 or L2.
28 Mc.: C2.

Asterisk: Resonances without wire loop.

DATA FOR FIGURE 2

Example: Indoor use.

- L1—7 turns, 37 mm. diam., 16 mm. long.

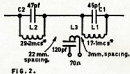
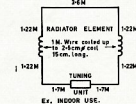


FIG. 2.

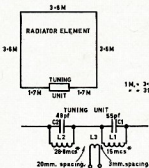


FIG. 1.

- L2—4 turns, 37 mm. diam., 16 mm. long.

- L3—4 turns, 37 mm. diam., 9 mm. long.

1 mm. copper wire was used for the coils.

Aerial Resonances S.W.R.

14.15 Mc.	1:1
21.23 Mc.	1:1.1
28.72 Mc.	1:1.3

Select reflector and director frequencies as usual. Spacing as for 21.3 Mc.

Capacitors: Ceramic 38 mm. diam., or pieces of co-ax. cable, 10 kva., NPO.

Fine tuning:

- 14 Mc.: Wire length or L1.
21 Mc.: C1 or L2.
28 Mc.: C2.

Asterisk: Resonances without wire loop.

—H. F. Ruckert, VK2AOU

☆

Integrated Circuit I.F. Strip

In the course of designing a transceiver I had occasion to build the i.f. strip as shown. It has certain features that may make it attractive for new projects or as an outboard addition to an older receiver.

It features high gain (37 db.), good stability, product detector or a.m. detector, operation from +12 volts, and limiting or a.g.c. if required.

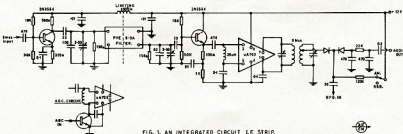


FIG. 1. AN INTEGRATED CIRCUIT I.F. STRIP.

WIRELESS INSTITUTE OF AUSTRALIA FEDERAL EXECUTIVE

The Institute can now offer annual subscriptions to the following Amateur Journals:—

- ★ "QST"—Associate membership and renewals, \$6.40.
- ★ R.S.G.B. "Radio Communication" (ex "The Bulletin") is only sent with membership of the Society. Send for application form and FREE sample copy of the R.S.G.B. "Radio Communication," \$5.50.
- ★ "CQ" Magazine, \$6.20.
- ★ "73" Magazine, \$4.50.

R.S.G.B. Publications and A.R.R.L. Publications available.

Send remittance to Federal Executive, C/o P.O. Box 36, East Melbourne, Vic., 3002.

The filter circuit is straightforward and uses the Pye 9-0A filter, which has a 4.5 db. insertion loss.

The main amplification takes place in the Fairchild's integrated circuit. This is an r.f./i.f. amplifier which is quite attractive in price. The coil is one of the ferrite slugs with a hexagonal hole through it, the wire being wound on toroidally, which results in a compact coil with high Q and little external field. A feature of the uA703 is that limiting is available if required, by merely arranging the turns ratio of the coil so that the effective load impedance is less than 3,300 ohms.

If a.g.c. is required current is bled from pin 5, using an external transistor as shown in the diagram.

The product detector is a simple one but quite effective if high back resistance diodes are used. In the a.m. position, varying the value of the 120K resistor may increase the efficiency of the detector, depending on the diodes used.

—I. Fyfe, VK2ZIF.

Single Sideband Transceiver Development in Australia

PRESENTED with the problem of designing sideband equipment as a commercial project, where would one commence? Who would be likely to have an interest in such a project? Where would you expect to find your markets? A small amount of thought gives as possibilities, the Armed Services, Civil Defence Services, Flying Doctor Service, Fishing Fleets, Amateurs and many others.

Having arrived at this point, is it possible to produce equipment adaptable to two or more of these services, if not in total, at least in part? Recognising the fact that the Armed Services have extremely sophisticated needs, let us for the moment leave them out of our consideration, and look at the requirements of such organisations as the Flying Doctor Service, fishing fleets and small craft. Here there are definite points where the requirements are similar and not entirely identical. These are the requirements for fixed frequencies. Power requirements may be similar and their frequencies not too widely spread. With little effort the one piece of equipment may be altered to suit the various services.

On the other hand, the needs of the Amateur call for something more complex. He will want to operate on three, if not five, bands with frequencies spread from 3.5 to 30 Mc. with the ability to operate on any frequency in a selected band, hence the transmitter and receiver must be tunable over each segment.

Just where should the designer start? No doubt various people would give various answers, some would suggest designing firstly the least complex piece

of equipment and eventually add the extra features required by the Amateur. Others may elect to design firstly for the Amateur with the object of scaling back to suit the services with fixed frequencies. This writer has no intention of advocating any particular approach to the many problems attached to the making of such a decision. He does, however, commend the efforts of an Australian company that has tackled the problem, and decided in favour of the Amateur equipment approach.

Having made the decision, the specific needs of the Amateur must be considered, and here there are probably as many ideas as there are Amateurs, and it becomes a case of meeting the needs of the greatest possible number at the most economical price. This problem is presented to the staff at the Technical Centre, Australian Consolidated Industries, Sydney. After months of work, specifications were agreed to, designs drawn up, and a large amount of developmental work done, up to the stage where a limited number of possible interested parties could be invited to a demonstration with the object of offering comments and suggestions. It was my good fortune to be included in the list of those invited, along with representatives of the Air Force, Civil Defence Services, Flying Doctor Service, P.M.G. Department, and selected trade publications.

A.C.I. TECHNICAL CENTRE

It could be, at this stage, that some readers know A.C.I. only by their slogan, "Good Things Come In Glass". For their benefit, the following brief

details of the Technical Centre are included:—

The Technical Centre, with 70 graduates in a staff of 225, is under the direction of Dr. A. Draycott, Manager, Technical Centre. It comprises four departments: Central Laboratories, Engineering Services Group, Central Design Office, and Technical Library.


Central Laboratories' staff presently number 125 including 50 scientists, 9 technical officers and 66 laboratory assistants. The Laboratories comprise:

Four Laboratories—

- (a) Physics Laboratory.
- (b) Inorganic Chemistry Laboratory.
- (c) Spectrographic Laboratory.
- (d) Fuel and Organic Laboratory.

Fourteen Research and Development Groups—

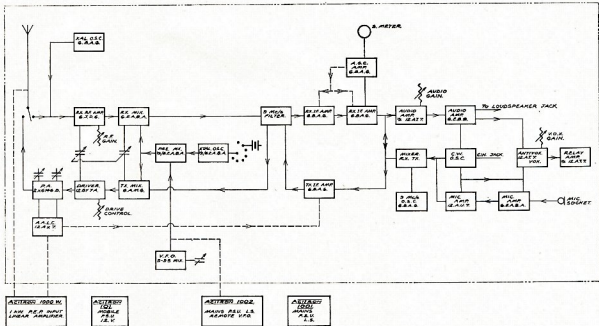- (a) Glass Technology Research Group.
- (b) Glass Physics and Chemistry Research Group.
- (c) Raw Materials (Geology) Research Group.
- (d) Surface Coatings Research Group.
- (e) Polymers Research Group.
- (f) Refractories Research Group.
- (g) Metallurgy Research Group.
- (h) Paper Research Group.
- (i) Packaging Research Group.
- (j) Chemicals Research Group.
- (k) Radiation Research Group.
- (l) Development Engineering Group.
- (m) Process Control and Electronics Group.
- (n) Technical Consultant.



Analytical Work.—Presently the regular analytical work amounts to an average of 1,200 analytical results issued every week. This is about one-third of Central Laboratories' effort.

Research and Development.—This represents about two-thirds of the effort, although this proportion will increase. Research covers an exceptionally wide range of disciplines, physics, chemistry, geology, metallurgy and chemical engineering. It also embraces many technologies, fuel, glass, plastics, food, polymers, paper, refractories and surface coatings.

Facilities.—The Laboratories are very well equipped, with a whole range of scientific apparatus, including photographic and direct reading spectrographs, U.V.-visible, I.R. and A.A. spectrophotometers, flame photometer, gas chromatograph, tensile and compression testing apparatus (Instron to 10,000 Kg, Avery to 50 tons), x-ray diffraction and fluorescence equipment, radiographic and α -irradiation facilities, mass spectrometer, differential thermal analysis apparatus, metallurgical and metallographic testing equipment.

DEMONSTRATION OF EQUIPMENT

The demonstration opened at 4.00 p.m. when Dr. Drycott welcomed the visitors and introduced Mr. John Bays (VK2BLH), Senior Development Engineer, Process Control and Electronics Group, who briefly outlined the purpose of the demonstration. This was followed by an inspection of the Technical Centre, to enable the visitors to gain an appreciation of the extent of the work undertaken, finishing in the electronics section where the equipment was described and demonstrated.

A large amount of interest was shown by those present and many questions were asked by those present. Although the demonstration and discussion was scheduled to finish by 7.30, it was after 10 p.m. before the informal discussion groups broke up and departed.

Although the exercise at present is to decide the feasibility of producing sideband transceivers with input powers of 200 and 600 watts p.e.p., a linear with 600 watts p.e.p. input, power supplies to match, and an s.w.r. meter, many other items of equipment, orientated towards the Amateur market were discussed.

Space does not permit us to publish full details of all items being developed, but the following details and block diagram will give some idea of the scope of the work so far done. These details cover the ACITRON 200W, which unit is considered most likely to find a ready market. The price indication is \$478 including sales tax, which compares favourably with imported equipment.

PROPOSED ACITRON 200W

This transceiver has been specifically designed for the Australian market, being a low cost, mobile or fixed station, five-band s.s.b./c.w. transceiver.

The Acitron 200W embodies the following features:—

- ★ Solid state v.f.o.
- ★ 80 to 10 metre coverage.

- ★ S.s.b. 200 watts input p.e.p.
- ★ C.w. 180 watts input.
- ★ High frequency crystal filter (9 Mc.).
- ★ Full coverage of all bands with 500 Kc. band segments.
- ★ Calibration to 1 Kc.
- ★ Backlash-free vernier control of frequency with direct frequency readout.
- ★ Built-in 100 Kc. calibrator.
- ★ Automatic peak level control.
- ★ Vox control.
- ★ May be used as a fixed or mobile operation with the appropriate power supply unit.

The Acitron 101 is a 12v. d.c. mobile p.s.u. and weighs ten pounds. Price \$150 complete.

The Acitron 1001 is an a.c. power supply incorporating a loudspeaker, and weighs twenty pounds. Price \$100.

SPECIFICATIONS FOR THE ACITRON 200W

Receiver—

Sensitivity: Less than 0.5 mV. for 10 db. signal to noise ratio of s.s.b. operation.

Selectivity: 2.1 Kc. at 6 db down, and 4.5 Kc. at 60 db down (9 Mc. filter).

Input: Low impedance for unbalanced co-axial inputs between 50 and 100 ohms.

Output: Low impedance to drive 5 to 10 ohms speaker and high impedance phone output.

Audio power output: 3 watts with less than 10% distortion.

Spurious responses: Image and i.f. rejection better than 50 db and internal spurious signal below an equivalent antenna input of 1 microvolt.

Transmitter—

D.c. power input: S.s.b. (A3J emission), 200 watts p.e.p. for normal voice continuous duty cycle; c.w. (A1 emission), 180 watts, 50% duty, tone generator monitor.

R.f. power output: 120 watts p.e.p. on 80, 40, 20, 15 and 10 metres into 50 to 100 ohms.

Spurious output signal: 60 db below rated output.

Harmonic radiation: 45 db below rated output.

Transmit/Receive operation: S.s.b. manual or vox, c.w. (vox from keyed tone on c.w.). C.w. tone internally switched to receiver a.f. amplifier for monitoring purposes in both the c.w. and tune-up position.

Microphone input: High impedance dynamic type.

Carrier suppression: Minimum 45 db down from single tone input.

Unwanted sideband suppression: Minimum 45 db down from single tone input at 1,200 cycles.

Third order distortion: 30 db down from two-tone output.

Peak level control: 10 db or greater at 0.1 milliamp. final grid current.

Frequency coverage: 3.5 to 4 Mc., 7 to 7.5, 14 to 14.5, 21 to 21.5, 28 to 28.5, 28.5 to 29 Mc.

Frequency stability: Drift less than 100 cycles per hour after 30-minute warm up from normal ambient temper-

ature conditions. Less than 100 cycles for a $\pm 10\%$ line voltage variation.

Modes of operation: Upper sideband 28, 21 and 14 Mc.; lower sideband 7 and 3.5 Mc.

Dial calibration: Every 1 Kc.

Dial mechanism: Backlash less than 20 cycles.

Calibrator: 100 Kc. crystal.

Audio response: 200 to 3,000 cycles per second within 6 db.

Front panel controls: Main tuning dial, driver tuning and pre-selector, final tuning, final loading, band switch, function switch, meter switch, gain control, audio gain control (on receive).

Side controls: Meter zero control, vox sensitivity, vox delay and anti-trip neutralisation, phone, and c.w. jack.

P.s.u. requirements: 12v. 9a, 240v. d.c. at 100 mA, 300v. d.c. at 30 mA, 800v. d.c. at 250 mA, 100v. d.c. at 20 mA.

Mobile Acitron 101 is designed for 12v. operation, positive or negative earth. Receive current 6 amps, transmit current 15 amps., continuous peaking to 35 amps.

The Acitron 1001 may be used for 110/230v. a.c. 50 to 60 cycles mains supply, incorporates a loudspeaker and a low impedance phone jack together with a manual transmit/receive switch.

It must be understood that the specification, as quoted, is only tentative and could be altered in the light of the discussions which followed the demonstration.

No attempt has been made to evaluate this equipment, as this would require much more time than was available at the demonstration, suffice to say that from what was seen and heard, a most favourable impression was obtained, and we hope to have the opportunity of making a more comprehensive examination and test at a later date.

★


ERRATA

Some mistakes appeared in the circuit diagram of "A Simple Low Cost High Voltage Supply" (March 1968 "A.R.") They were:—

- (a) D5 was drawn in back to front.
- (b) The OB2 was also drawn in back to front.

As the circuit is shown, the output would be positive instead of negative. This could cause the 100 μ F. capacitor to short circuit and in turn cause D5 to burn out.

The corrected circuit is shown below.

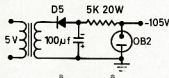

In the July issue of "A.R." (page 8) the article, "Adapting the Geloso G209 for S.s.b. Reception," was submitted by Ron Fisher, VK3OM. It is regretted that his name was omitted.

Join in the Victorian 160 Metre Contest

In order to promote activity on 160 metres, the Victorian Division of the W.I.A. has organised a contest, the rules being given below. The contest is open to all comers, and we hope to receive logs from all States. Note that cross-band operation is permitted, so you can join in the fun even if you have no transmitting equipment for 160.

RULES

Purpose: To encourage greater occupancy of the 160 metre band.

Dates and Times: 1200 E.A.S.T., Saturday, 5th October, 1968, to 1200 E.A.S.T., Sunday, 6th October, 1968.

Band: 160 metres—1.80 to 1.86 Mc. Cross-band operation is permitted.

Modes: All authorised modes may be employed, and cross-mode operation is permitted.

Logs as follows:

Date/ Time E.A.S.T.	My Freq. Band	His Freq. Band	Call Sign Sta'n Work.	No. Sent	No. Rcvd.	Points Claim.

Exchanges: RS(T) followed by three digits, commencing at 001.

Scoring: Stations may be contacted once during each calendar day and scores claimed for each of those contacts.

Stations may count, for scoring purposes, pre-arranged cross-band contacts, but not pre-arranged 160 metre band contacts.

160 Metre/160 Metre contacts:

Fixed (5 pts.) to fixed (5 pts.).

Fixed (5 pts.) to Portable/Mobile (10 pts.).

Portable/Mobile (10 pts.) to Portable/Mobile (10 pts.).

160 Metre/Cross-band contacts:

160 mx fixed (5 pts.) to fixed (5 pts.).

160 mx portable (10 pts.) to fixed (5 pts.).

160 mx portable (10 pts.) to portable (5 pts.).

160 mx fixed (5 pts.) to portable (5 pts.).

A bonus of 20 points may be claimed for each interstate contact, and a bonus of 30 points may be claimed for each overseas (DX) contact.

A bonus of 20 points may also be claimed for contacts make from a Victorian National Park.

A multiplier of 1.5 may be applied to the score for the use of a power input of less than 10 watts to the final stage.

Listeners: 10 points per contact heard on 160 metres.

Entries: Logs must be returned to the Admin. Secretary, Victorian Division, P.O. Box 36, East Melbourne, Vic., 3002, by Friday, 1st November, 1968.

Awards: At the discretion of the Council of the Victorian Division of W.I.A., the following awards may be made:

VK3 Stations—

Highest score: (a) Fixed, (b) Portable/Mobile.

Second highest score: (a) Fixed, (b) Portable/Mobile.

Highest Listener's score.

Others Stations—













Highest score in contacts with VK3 stations.

AMATEUR FREQUENCIES:

ONLY THE STRONG GO ON—
SO SHOULD A LOT MORE
AMATEURS!

PREDICTION CHARTS FOR SEPTEMBER 1968

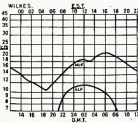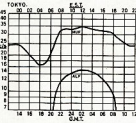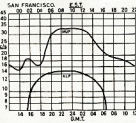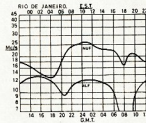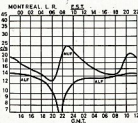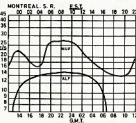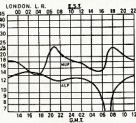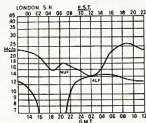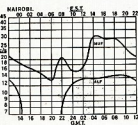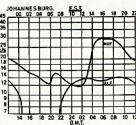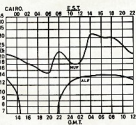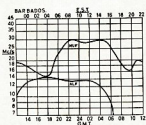(Prediction Charts by courtesy of
Ionospheric Prediction Service)



Field Day Fun—or—Heat, Flies and Donga

SITUATED approximately 130 miles north-west of Port Augusta is an area at times featureless, rock strewn and generally quite inhospitable. This is South Australia's far north, and usually considered only good for running a few sheep. Acres to the sheep incidentally, not sheep to the acre. Trees are few and far between and then only a form of stunted growth.

Into such an area my associate in the Field Day, Ron Thrum, a keen S.W.I., and myself set off to establish a portable station.

The first problem, having sorted out the matter of equipment, was to make it to the selected site. This was on the old road to the opal mining town of Andamooka on the south-east edge of a hill overlooking the Commonwealth Railways siding of Wirrappa.

A week or so previously the area had received an unexpected 2 inches or so of rain (annual average 7 inches) which really "does things" to the dirt roads. The top-soil has a high clay content and water will lie in pools for weeks after such a downpour. So, somewhat dubious as to how we'd go, we began our little trip.

WHERE'S THE ROAD?

Three choices of track were available with two entry points quite close. The first of these two looked quite promising for the first 800 yards, but then across the transcontinental railway line and onto a gluey surface. A continual slide for the next 500 yards, a bend negotiated and then where is the road? (track?) The path is identified by saltbush edges and consisting of loose rocks was discernible, so "press on" was the order of the day.

Several hundred yards of this and it was deemed advisable to keep going, "It might improve!" However, the rain coming down the side of the hill had done a thorough job and the rocks gave way to boulders strewn everywhere and weighing anything up to 300 lbs. With the wheels coming up against these, it was often necessary to back a little and lever them out of the way.

With Ron selecting the most likely path, shouted instructions, loud and slightly naughty words (no one around for miles), more levering and with a sharp drop on one side, we continued seemingly ad infinitum, climbing all the while to make the top of a crest. This took about half an hour at a maximum speed of nearly 2 m.p.h. Then down the hill, turn left at the bottom, then climb for about three miles quite steeply.

But! Down the hill was the same and at the bottom the creek had flowed quite swiftly, allowing about two inches to spare each side of the wheels, still wet and slippery, with a two-foot drop one side and easy four feet the other. Bottom gear, eyes closed and

gun the motor, hit the brakes, fortunately power type, and a big sigh of relief. Up the hill in reasonable comfort as the water had run directly down, producing mere furrows. All of 15 m.p.h. now at times.

The spot was located next to a large concrete water tank about 30 feet high and 300 feet across with a ladder to the top. This is on the pipe line. Dipoles were strung from the top rail of the ladder with the other end anchored on the ground with, you've guessed it, rocks.

Our bottles of cool drink were attached to wires and lowered into the water tank to a depth of 20 feet or so. The radiator was also filled from this source at an opportune moment.

EQUIPMENT

This comprised a petrol generator set placed about 300 feet away to reduce interference problems, none encountered from this unit anyway, an FL100B transmitter and my much worked over AMR300 receiver. Suffice to say, this combination performed admirably for the duration of the contest.

While daylight lasted it was considered advisable to try the alternative route out. A sked with KX6FJ also necessitated a return to base where the beam was available, not to mention dinner awaiting us at home.

ANOTHER TRACK OUT

After disconnecting antennae and power feed, packing tx/rx, and a false start down a wrong track, we were away. All okay till we came over the crest. Here again the water had run down the steep slope but the furrows, up to three along the length of the road, had been gouged out to depths of about four feet in places and had to be straddled, with similar drops each side. However, just a matter of care and slow going.

Down on the flat all was well, as running in loose sand is a common experience. A still-running creek only inches deep forded and then, no, not more rocks, but a dry creek bed. The water had rushed down this so swiftly

it had thrown up a sandbank about four feet high on our side and also left a sandy bed. Digging wheel tracks through the sand bank and levelling it off provided an approach with merely two-foot banks to negotiate. Here the abundance of rocks saved the day, although we exhausted the supply of flat ones in that locality in building our bridge.

On to the main road and our evening sked made with minutes to spare.

With Ron busy for the evening, I returned to the site for several hours, using our latter route without further misadventure. The road never looks as bad at night. Back home again, and the soft bed felt luxurious.

COME THE CONTEST

Next morning back for the long stint, this time also equipped for the heat with more soft drink and a large vacuum flask filled with cordial and lovely big ice cubes. A mistake! The insides of such flasks are not designed to have ice blocks slammed against them. We managed to salvage the ice and didn't cut our mouths on any broken glass.

Into operations again, but with the station wagon closed up, we dripped perspiration, and with doors and windows opened we were besieged by the friendliest of flies! This was dealt with by alternating the two states of being and copious application of insect repellent and fly spray, of which we made sure we had an abundant supply.


I might add that the temperature can climb to pretty high figures in this area, but swimming is not allowed in the water tanks!

But the contacts came along and we really enjoyed ourselves throughout the contest. Hope to see you in it again next year, 1969.

By the way, any requirements for rocks can be easily met on demand, F.O.R. to your nearest railway station, and if you're driving to Andamooka we'll forward snaps for the best route by air mail.

—Ian VK5QX/P.

CHOOSE THE BEST—IT COSTS NO MORE

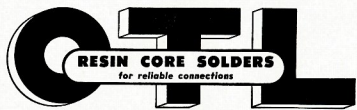

O. T. LEMPRIERE & CO. LTD. Head Office: 31-41 Bowden St., Alexandria, N.S.W., 2015
and at Melbourne — Brisbane — Adelaide — Perth — Newcastle

NEW CALL SIGNS

MAY 1968

VK1RY—F. W. N. Ryan, Station: 47 Cockle St., O'Connor, 2041; Postal: P.O. Box 43, Canberra, 2600.

VK1ZOO—J. A. Gardner, Reid Hotel, Allora St., Canberra City, 2601.

VK1LH—L. Pearson, 8 Rawson Rd., Berowra, 2081.

VK1RA—R. A. Priddle, 34 Cleveland St., Wahroona, 2076.

VK1AB—B. S. Sullivan, 21 Chief St., Belmont, 2280.

VK1AE—B. L. Mills, 15-17 Coral Rd., Cronulla, 2230.

VK1BD—D. A. Bolton, 115 Terry St., South Hurstville, 2220.

VK1BDK—D. Lee, 95 Seafarth Cres., Seafarth, 2092.

VK1BG1/T—J. Gray, 121 Cardiff Rd., South Wolland, 2287.

VK1BJ—B. J. Booth, 2 Ethel St., Burwood, 2134.

VK1BK—S. A. Knowles, 22 Rainbow Pde., Penkese, 2072.

VK1BL—B. J. Bay, 30 North East Cres., Lilli Pilli, 2229.

VK1BNA—A. Nutley, 32 Clarke St., West Ryde, 2114.

VK1BOD—O. M. Duffy, 83 Viking St., Campsie, 2194.

VK1BTP—P. Richardson, 37 Fourth St., Dapto, 2530.

VK1BTN—R. N. Threlfo, Station: 105 Roxburgh St., Stockton, 2295; Postal: P.O. Box 10, Newcastle, 2280.

VK1BUA—U. H. Aalbers, 687 Pemberton St., Albany, 2640.

VK1ZCO—C. M. Covelade, 18 Sorrell St., Parramatta, 2150.

VK1ZDE—D. A. Cliff, Station: 182 Rusden Rd., Blaxland, 2774; Postal: P.O. Box 10, Katoomba, 2780.

VK1ZJG—J. Holt, 62 Mepunga St., Concord West, 2138.

VK1ZMW—W. G. Penman, 39 Tobruk Cres., Orange, 2800.

VK1ZPJ—R. F. Jackson, 26 Ada Ave., Wahroonga, 2076.

VK1ZT—J. Thompson, 2 Gow Ave., Albion Park Rail, 2527.

VK1ZZA—A. C. M. Anderson, 32 Oak Rd., Wattle, 2230.

VK1ZYB—G. K. Chapman, 11 Bayswater Rd., Roseville, 2069.

VK1CR—A. A. Andros, 502 High Street Rd., Mt. Waverley, 3149.

VK1HB—H. H. Baker, 7 Kara St., Doncaster East, 3109.

VK1QW—P. R. Forbes, 44 Hamel St., Box Hill, 3102.

VK1ZP—P. N. Engelmann, 65 Allmar Rd., Glen Waverley, 3150.

VK1TX—D. R. Blackman (Dr.), 129 Clayton Rd., Clayton, 3168.

VK1WA—M. A. Webb, 10 Fran Cres., Rosanna, 3084.

VK1AAU—G. H. Gaspara, 23 Hudson St., North Caulfield, 3161.

VK1AOT/T—R. J. Halligan, 41 Windsor Ave., Mt. Waverley, 3149.

VK1AQ1—M. C. Mann, Mortlake Rd., Warrnambool, 3280.

VK1AQ2—D. I. Ralph, Flat 4, 58 Chestnut St., Victoria Park, 3211.

VK1AQR—D. R. St. John, 7 Coquette St., West Geelong, 3218.

VK1AQY—W. T. Moffat, 83 Mathoura Rd., Tootell, 3142.

VK1ASQ—M. R. Trickett, 8 Matlock St., Herne Hill, 3218.

VK1AUP—H. Beedle, Flat 21, 41 Northcote Ave., Caulfield, 3162.

VK1AVO—M. H. G. Evered, 13 Sage St., Oakleigh, 3166.

VK1AWR—W. E. Knapp, 35 Alandale Rd., Blackburn, 3130.

VK1AYY—C. J. D. Smith, 80 Beaver St., East Melbourne, 3002.

VK1AAE—A. P. J. Radio Club, Gillies St., Wendouree, 3325.

VK1ZAP—E. C. Lawson, Station: Kelvin Gr. Cherry Tree via Sebastopol; Postal: P.O. Box 1, Sebastopol, 3306.

VK1ZDY—C. J. Lefel, 24 Chippewa Ave., Mitcham, 3219.

VK1ZEO—E. N. Fattie, 7 Boyne St., Geelong East, 3219.

VK1ZGO—R. G. Rowlands, 35 Cratloe Rd., Geelong East, 3219.

VK1ZGL—J. J. Kennedy, 15 Cook St., Newtown, 3220.

VK1ZJB—J. B. Charles, 156 Melbourne Rd., Williamstown, 3016.

VK1ZKT—R. A. Eldred, 50 Day St., Balmaleale, 3075.

VK1ZKY—R. G. O. Wilson, 45 Pleasant Rd., Hawthorn East, 3122.

VK1ZLZ—L. W. Cox, 30 Belford St., Ballarat East, 3350.

VK1ZMU—M. H. Reynolds, 4 Balmoral Ave., Kew, 3101.

VK1ZQO—M. J. Hayes, 68 Kerferd St., East Malvern, 3145.

VK1ZQO—A. B. Bradley, 23 Langdon St., Forthlington, 3223.

VK1ZQG—J. H. Gras, 8 Stone St., East Brighton, 3187.

VK1ZGY—G. G. Hepler, 43 Bellarine St., Geelong, 3220.

VK1ZGZ—G. D. Weymouth, 11 Kirkwood St., Eaglehawk, 3556.

VK1ZTF—P. J. Fitzherbert, 9 Studley Ave., Bendigo, 3556.

VK1ZUN—B. S. W. Churchill, Flat 3, 3 Barnaby Rd., South Yarra, 3141.

VK1ZVQ—D. A. Evans, 6 Vila Crt., Oakleigh, 3180.

VK1ZKU—D. K. Freeman, 64 Vicki St., Forest Hill, 3131.

VK1ZVU—U. H. Clarke, 23 Glen Dr., Eaglemont, 3084.

VK1ZZF—P. L. Bell, 11 Berkeley St., Hawthorn, 3122.

VK1ZZI—G. J. Greenwood, 9 Grundy Gr., Pascoe Vale South, 3044.

VK1ZZJ—J. E. Westernman, Flat 7, 19 Sydney St., Melbourne, 3183.

VK1ZZQ—T. P. Mitchell, 4 Grant St., Newtown, 3200.

VK1ZZY—F. J. Fitzwater, 49 Claremont Ave., Malvern, 3144.

VK1RT—R. H. Cost, 14 Jellicoe St., Coorparoo, 4151.

VK1UA—D. R. Clark, 182 Hornibrook Exp., Clontarf, 4019.

VK1ZET—E. J. Morris, 210 Hume St., Too-woomba, 4250.

VK1ZNP—N. N. Potts, 19 Mayrene St., Carina, 4250.

VK1ZRW—A. A. Wilson, 45 Atherton St., Edge Hill, 4370.

VK1ZTA—G. T. Adamson, 3 Maker St., Too-woomba, 4250.

VK1ZVN—V. G. Novotny, 78 Dorrigo St., Kedron, 4031.

VK1SDV—N. K. Kohler, 15 Jury Ave., Rose-treavor, 5073.

VK1SHU—H. L. Gillon (Dr.), 7 Ella St., Park-side, 5055.

VK1KNO—L. H. Vale, 29 Calton Rd., Gawler, 5118.

VK1KTP—T. Roberts, 10 West Beach Rd., West Beach, 5024.

VK1ZAY—K. R. Bone, 23 Mackay Ave., Plym-pton, 5038.

VK1ZGI—G. J. Thomas, 4 Staehr St., Nuri-coutpa, 3355.

VK1ZGN—D. L. Park, 1 Rosedale Ave., Morphettville, 5043.

VK1AQ—G. R. Crews, Naval Communications Station, Ennough, 5097.

VK1JA—B. J. Arbon, Stone St., Borden, 6338.

VK1ETT—T. P. Taylor, 67 Central Rd., Rossmoyn, 6155.

VK1ZBW—R. S. Savill, 65 Action Ave., River-vale, 6103.

VK1ZBZ—B. Weir-Smith, 24 Knox Cres., Mel-bourn, 6104.

VK1ZDQ—M. E. Zille, 187 Campbell St., Bel-mont, 6104.

VK1ZEB—B. N. Brooks, 85 Shaftsbury Ave., Bedford, 6052.

VK1ZEH—H. E. Christensen, 65 Federation St., Mt. Hawthorn, 6016.

VK1ZLT—L. F. Tossaint, 19 Errinbee St., Riverton, 6155.

VK1GH—G. L. Hall, 54 Clare St., New Town, 7008.

VK1TKK—T. K. Emmett, 6 Haig St., Lenah Valley, 7008.

VK1ZLC—L. C. Dean, 47 O'Brien St., Glen-orchy, 7010.

VK1HR—R. Hester, Station: Tanga St., Kavleng, N.G.; Postal: C/o Electricity Commission, Kavleng, N.G.

VK1J5—J. B. Eacey, Ukurumpa, E.H.D., N.G.

VK1UC—Ukurumpa Radio Club, Station: Ukurumpa, N.G.; Postal: P.O. Ukurumpa, E.H.D., N.G.

CANCELLATIONS

VK1GT/D—D. A. Page, Transferred to Vic.

VK1ADV—C. M. Hicks, Not Renewed.

VK1BIC—G. Kempton, Not Renewed.

VK1ZCW—C. H. Wall, Transferred to N.T.

VK1ZBIS—J. B. Bay, Now VK1ZJG.

VK1ZJG—T. J. Gray, Now VK1BG1/T.

VK1ZLD—L. W. Doolan, Not Renewed.

VK1ZPQ—J. A. Gardner, Now VK1ZOO.

VK1JHY—H. L. Andrews, Deceased.

VK1AED—D. A. Connelly, Deceased.

VK1JAK—W. B. Brain, Transferred to Willis Island.

VK1AJL—J. F. Long, Deceased.

VK1ZEP—P. N. Engelmann, Now VK1ZQW.

VK1ZGZ—J. W. Monro, Not Renewed.

VK1ZJB—B. H. Baker, Now VK1HBD.

VK1ZJV—J. H. Van Den Breuk, Not Renewed.

VK1ZNC—D. R. St. John, Now VK1AQ1.

VK1ZNF—M. R. Trickett, Now VK1ASQ.

VK1ZOL—M. G. Foster, Transferred to Qld.

VK1ZPS—D. R. Blackman (Dr.), Now VK1ZTX.

VK1ZRD—J. B. Charles, Now VK1ZJB.

VK1ZVF—G. H. Gaspara, Now VK1AAU.

VK1ZUC—E. J. Coan, Returned U.S.A.

VK1ZUC—H. H. Cost, Now VK1RT.

VK1ZHB—F. J. D. Freese, Cashed Operation.

VK1ZBL—B. A. Endersbee, Transferred to Vic.

VK1ZEL—B. J. Arbon, Now VK1JA.

VK1ZFP—D. J. Freese, Cashed Operation.

VK1ZAO—T. R. K. Emmett, Now VK1TKK/T.

VK1ZNO—L. H. Vale, Now VK1KNO.

VK1ZGC—A. Sandilands, Now VK1ZGC.

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. Position in the list is determined by the first number shown. This first number represents the participant's total countries less any credits gained for deleted countries. The second number shown represents the total D.X.C.C. credit gained including deleted countries. Where totals are the same, listings will be alphabetical by call.

Credits for new members and those whose totals have been amended are also shown.

PHONE			
VK3MS	317/338	VK3AB	300/314
VK3AHO	314/328	VK4FJ	284/301
VK6RU	307/330	VK4TY	277/278
VK3JMK	304/321	VK3JMK	271/275
VK2JZ	303/318	VK2APK	264/267
VK4HR	302/318	VK2AAK	263/267
New Members:			
Cert. No.	Call	Total	
85	VK3BB	116/119	
86	VK4MY	172/172	
87	VK4UC	106/106	
Amendments:			
VK4KS	297/183	VK4PY	153/153
VK3ZE	189/193	VK3AMK	137/137
VK3SM	161/184	VK3AGH	110/120

VK3QL	302/322	VK3ARX	267/275
VK3AHQ	294/306	VK3NC	266/266
VK3JC	281/312	VK3YL	265/262
VK4FJ	291/313	VK6RU	264/265
VK3AGH	282/295	VK3XB	263/276
VK4HR	274/296	VK2APK	261/268

New Member:			
Cert. No.	Call	Total	
93	VK4MY	111/111	
Amendments:			
VK4TY	255/266	VK3KS	219/225
VK4UC	253/253	VK3AX	154/162
VK3RJ	242/255	VK4KS	131/136
OPEN			
VK2AGH	311/329	VK4FJ	228/320
VK4HR	309/323	VK3EO	220/214
VK3RU	309/322	VK3ARX	220/226
VK2VN	306/321	VK3CT	227/281
VK3MK	305/322	VK2APK	226/282
VK4TY	303/315	VK2ACX	276/300

W.I.A. H.A.-VK-C.A. AWARD (S.W.L.)

Listed below are details relating to those Overseas Ways Letters to whom this Certificate has been awarded.

Cert. No.	Call	Date Awarded
1	SM0-2086	9/11/66
2	UA0-29108	21/11/66
3	UA9-9849	11/7/67
4	W2-6893	27/7/67

Correspondence

Any opinion expressed under this heading is the individual responsibility of the writer and does not necessarily coincide with that of the Publishers.

MORSE PROFICIENCY

Editor "A.R.," Dear Sir,
I refer to the statement by Alan Shawsmith, VK4SS, in "A.R." for June, dealing with Morse proficiency.

The following are a couple of points which might further aid learners:—

Firstly, do not try to spend too much time at it once.

In the course of his training of R.A.A.F. recruits during the war, the late Merv. Brown, VK5MR, found that at the end of half an hour his class could absorb no more and the balance of an hour's lesson was not productive. He evolved the idea of seven minutes Morse and a three-minute break. This was filled in with music, to change the train of thought perhaps. Suffice it to say that "authority" frowned until Merv. was able to show that, by giving six periods of 7 minutes each, to equal 42 minutes, he was doing more good with the trainees than under the old method. It was then approved. My authority for this was Merv. himself, about 1951.

Secondly, when you start sending (and this is not recommended until you can recognise sounds as characters at about 10 w.p.m.) keep the bar of the key and forearm in a straight line. This avoids wrist strain and, having had it improve on me in my youth, I can assure you my wrist is still okay after 50 years of it. It is all wrist work in my book.

I think it advisable that a learner should be fully aware of what good signals sound like before he attempts to make any; otherwise how will he know what to try and make.

Experience also shows that a good Morse operator is less likely to other people's errors when using telephony, but, despite comments otherwise, taking messages by telephony is slower than by Morse, given reasonably good operators.

—T. Leidler, VK5TL.

QSL FOR W6QJN/MM

Editor "A.R.," Dear Sir,
For the past several months I have been trying to get a message across to VK Amateurs and therefore trust you can find space to publish my letter.

For several years I have been a very close friend and shipmate of James Quirk, W6QJN, who was the radio officer of the U.S.S. African Star, and I was with him as Chief Officer and more or less the second Amate operator. The day after the African Star, that the African Star was on the U.S. to Australia run, Jim made a lot of friends and I had the pleasure of meeting many of them also.

On 16th March, 1968, at 4 a.m., the African Star was proceeding down the Mississippi River on her way to the Gulf of Mexico. She was involved in a collision with an oil barge. As fate would have it, I happened to be on my annual inspection of Jim and the other crew members were lost or missing, and 20 crew members hospitalised. Just about three months after the collision, Jim's body was found. I am pleased to say there were several of his Amateur friends able to attend his funeral, but I was on my way to Australia and therefore unable to attend. He died of the collision, and in deep respect to Jim and other shipmates lost in this collision, every time I am on a ship passing the spot where the collision happened, the American flag on the stern of my ship will be lowered half mast.

Jim had not been an Amateur very long, but in the year that he was through the ranks of Jim VK4VMW had some QSL cards made up, showing the U.S. African Star on her way out of New York Harbour.

At the time of Jim's death there was close to \$5,000 worth of Amateur and electronic gear, and his log book, on board. It is now my understanding that this gear and log book have fallen into the wrong hands, and we may never see the log book again.

If you, A.R., will write to me, giving the date that he worked Jim, I can refer to my personal records and will be able to tell you the African Star was on that date. At the present time that is the only way I have to verify a QSO with Jim, and I will be glad to send a QSL card of Jim's. However, I must stress that it is the only way matter of some months before they get a card as I will not be returning to the States to my QSL card until the September. I am unable to leave the States again at any time.

One other method of verification is if they can show where they were in QSO with Jim and Newt. W1BCB and Ralph K0YTM.
My home QTH is: Box 87, Upper Fairmount, Maryland 21891, U.S.A.

—Charlie Carroll, W3NKCQ/MM.

TEMPORARY EMPLOYMENT IN NEW GUINEA

A limited number of vacancies exist for temporary employment as Radio Technicians with the Posts and Telegraphs, Papua and New Guinea.

The applicant should be qualified to take charge of a radio telephone station containing both h.f. and v.h.f. communication equipment.

Most of the stations are operated by only one technician who is responsible for maintaining the services in operation as required. Frank and telegraph offices are provided by a h.f. network but there are a few v.h.f. systems providing junction routes and exclusive subscriber services. The out-station network consists of a basic station, a radio transmitter and receiver while the out-stations operate on low powered transceivers.

The out-stations are grouped into zones. The Department also maintains broadcasting facilities for the Department of Information and Extension Services.

Applicants must have technical qualifications consist of communication transmitters used after hours for broadcasting services.

I am a retired P.M.G. engineer and have been requested to contact suitable technicians who would be prepared to spend a year or two in the Territories.

Applications for technical personnel from areas such as the private radio industry or the services would be considered.

Qualifications are completion of an approved course of training in radio telecommunications.

Pay will be at the rate of \$3,000-\$5,000 per annum. Salaries quoted are for single men and include allowances. Married men receive additional allowances for dependants. Income tax is at present about half that payable in Australia.

The period of employment preferred is for a two-year term. Successful applicants would work for 21 months then would be entitled to three months' leave pay and return air ticket.

I would be pleased to hear from those interested so that we could discuss the accommodation and local conditions.

—G.A. Wiffen.

Youth Radio Clubs Scheme of Australia

The first National Conference of the Youth Radio Clubs Scheme of Australia was held in Melbourne on Saturday, 1st June, 1968, at the rooms of the Victorian Division of the Wireless Institute of Australia.

A great deal of preliminary work had gone into the organisation of the Conference by the Youth Radio Clubs Scheme of Australia, Victorian Division, and this was an outstandingly successful conference.

Visiting delegates were treated with generous hospitality and provided with a most interesting time. The members of the Victorian Division regretfully left for their home States.

The purpose of the Conference was to organise the State groups on a national basis, to ensure uniformity of syllabuses, certificates and exchange of the VK call area.

The representatives were:
Mr. J. Battick, W.I.A., Federal President.
Mr. R. Black, Past Federal Supervisor.
Mr. R. Emmett, State Supervisor of Tas.
Mr. E. Ryan, W.I.A., Divisional President.
Mr. R. Guthrie, State Supervisor of S.A.
Mr. D. Jones, State Supervisor of N.S.W.
Mr. P. Plummer, W.I.A., Divisional President.
Mr. D. Reid, Editor of "Zero Beat".
Mr. H. Rider, Past State Supervisor of Vic.
Mr. H. Smith, Exam. Officer for Vic.
Mr. W. Tremain, Supervisor of the Correspondence Section.

Mr. J. Webster, Federal Co-ordinator to the W.I.A.

Apologies were received from both Queensland and Western Australian Divisions.

The meeting was opened at 14.22 hours with Mr. K. Pincott, W.I.A. representative, as chairman. State Supervisors had voting rights, and remaining members present acting in an advisory capacity in their own special departments.

Mr. Pincott welcomed all delegates to the conference on behalf of the W.I.A. and expressed the wish that most of the apparent differences between the various State groups would become settled to the complete satisfaction of all concerned.

Mr. Jones spoke of the N.S.W. Committee, regarding the youth radio club members could not be present but would be eagerly looking forward to their delegate's reports. He expressed the opinion that the conference would achieve an important but unwritten object—that of understanding the views and problems of other Divisions.

Mr. Plummer explained how the agenda had been drawn up and how all Divisions had been approached for their views regarding the items to be included on that agenda.

The business of the Conference then began with a lively discussion of the present position of the Youth Radio Scheme. The Scheme had begun quietly some years before as a means of providing inducements in the form of certificates, for members of Radio Clubs in Schools and other youth organisations.

The Scheme was adopted by the Wireless Institute of Australia to spread its educational activities. By now, it had grown into a rather

large, if sometimes clumsy, youth group, and it was felt that it might take a greater responsibility for its own affairs as an organisation affiliated with the W.I.A.

A motion moved by VK5 and seconded by VK4, that "the name of the organisation be the Youth Radio Clubs Scheme of Australia" was carried unanimously. With this motion, the Youth Radio Clubs Scheme of Australia was formally established.

Some fifteen motions were passed during the rest of the Conference, all designed to place the new organisation on a sound basis. Briefly, they provided for the drafting of a constitution for the Youth Radio Clubs Scheme of Australia, the appointment of a Federal Co-ordinator, the formation and administration of the Correspondence Section, the formation of a Syllabus, Standards Committee, acceptance of syllabuses at present in use by the Victorian Division, recognition of "Zero Beat" as the official publication of the Youth Radio Scheme of Australia, that the notes for the Elementary Junior and Intermediate Certificates be printed and distributed by the Victorian Division, and that a Federal Convention be held during 1969.

Included was a motion to create Mr. Rex Black a Life Member of the Youth Radio Clubs Scheme of Australia in recognition of his services to Y.R.S.

All motions were carried unanimously.

The Conference closed at 20.12 hours on Sunday morning and later the same morning much later, resumed at the home of Mr. Michael Plummer to prepare groundwork for the Constitution.

Do these changes affect the members of a Radio Club which is a member of the Scheme? No. The Syllabus Committee will make minor alterations in the present syllabuses. The Federal President of the W.I.A., Mr. J. Battick, stated that the Institute would at all times continue to assist the Youth Radio Clubs Scheme of Australia by supplying certificates, meeting facilities, etc. The State Supervisors are the person in each State who will do the main job of organising as previously and a committee will be appointed to help him in the larger States.

Those who attended the Conference came away satisfied that the Youth Radio Clubs Scheme of Australia was at the start of a new and important phase.



SSB EQUIPMENT

Yaesu Series—

Receivers: FR-50, FRDX-400.
Transmitters: PL-50, PLDX-400.
Transceivers: FT-50, FTDX-100, FTDX-400.
Linear Amplifier: FLDX-2000.

TH6DX Hi-Gain Tri-band Beam, \$199 each.
Mobile Whips (v.h.f.), from as low as \$5.
V.h.f. Beams from \$12. 2 m Ground Planes \$10. PL-229 and 80229 Type Connectors, \$8c each.

K-100 50/75 ohm Kyoritsu SWR Meters, uses amphenol type PL-229 connectors, \$20 each.
FP30-DX 3-section Low Pass Filters, takes PL-229 plugs, \$18.50.

P.T.T. Microphones (crystal, dynamic and ceramic). Mic. "curly" cords.

Amphenol type co-ax. plugs, sockets, angle adaptors, cable junctions, etc.

All prices Amateur net, inc. S.T. Freight and postage extra.

Bail Electronic Services

60 SHANNON STREET,
BOX HILL NORTH, VIC., 3129
Phone 88-2213

COMMUNICATIONS SERVICE TECHNICIAN

An Electronics Technician, experienced in the servicing of Solid State equipment, is required for the installation and maintenance of our Multitone Radio Paging systems.

The successful applicant would be provided with a vehicle, as some on-site servicing is required. A generous salary is envisaged for the right man and a superannuation scheme is available after a qualifying period.

Applications will be treated in confidence and should be made in writing to:

THE MANAGER,
WATSON VICTOR LTD.
201 VICTORIA PARADE,
COLLINGWOOD, VIC., 3066

Responsible

Electronic Technician wanted for assembly of specialised equipment

Must be experienced and preferably have qualifications equivalent to R.M.J.T. Technician's Certificate.

Apply to

AEGIS PTY. LTD.

347 Darebin Road, Thornbury,
Vic., 3071 Phone 49-1017

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)

Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)

Telegrams: "Metals," Adel.

Stockists of Radio and Electronic Components for the Amateur Constructor and Hobbyist

First Ring, Write or Call on

WILLIAM WILLIS & Co. Pty. Ltd.
430 Elizabeth St., Melbourne. Ph. 34-8539

Repairs to Receivers, Transmitters;
constructing and testing: xtal conv.,
any frequency; Q5-ers, R9-ers, and
transistorised equipment.

ECCESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 80-3777

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT

Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE
AVAILABLE IN FT243 HOLDERS:

6280, 4095, 4535, 2760, 2524 Kc.

5,500 Kc. T.V. Sweep Generator Crystals, \$7.25;
100 Kc. and 1000 Kc. Frequency Standard, \$17;
plus Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, \$13 each plus Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 Mc. AND 7 Mc. BAND.

Commercial—0.02% \$7.25, 0.01% \$7.55, plus Sales Tax.

Amateur—from \$6 each, plus Sales Tax.

Regrinds—Amateur \$3, Commercial \$3.75.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carell, Box 2102, Auckland.

Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

LOT 6, EILEEN ROAD, CLAYTON, VIC.

Phone 546-5076

With the co-operation of our overseas associates our crystal
manufacturing methods are the latest.





TRIO

SSB transceiver

200 watts PEP—7 Bands—A M & C W
and
Power Supply and Speaker Unit



PS 500 AC

TS 500

SPECIFICATIONS:

Frequency: 80m Band 3.5-4.0 MHz
40m Band 7.0-7.5 MHz
20m Band 14.0-14.6 MHz
15m Band 21.0-21.6 MHz
10m A Band 28.0-28.6 MHz
10m B Band 28.5-29.1 MHz
10m C Band 29.1-29.7 MHz

Communication Method: SSB (A3)
AM (A 3H)
CW (A1)

Maximum Input Power: (Xmitter final stage)
200W (PEP)

Standard Input Power: (Xmitter final stage)
180W (PEP) 120W on 28 MHz band only

Antenna Input Impedance: 50-75 ohm

Carrier Suppression Ratio: More than 40 dB

Single Side Band Ratio: More than 40 dB

Mic. Input Impedance: High impedance
(dynamic or crystal mic. recommended)

Xmitter Audio Frequency Characteristics:
300-3,000 Hz (-6 dB)

Receiver Sensitivity: 1µV S/N 10 dB
(14 MHz)

Receiver Selectivity: 2.7 kHz (-6 dB)
5.0 kHz (-55 dB)

Spurious Rejection Ratio: More than 45 dB

Image Ratio: More than 60 dB

Undistorted Power Output: More than 1W

Receiver Output Impedance:

SP 500 ohm

PHONE 8 ohm

Power Consumption (using PS-500AC):
450W (At maximum power output)
250W (Receiving Mode)

Tubes and Transistors used:

17 TUBES, 3 TRANSISTORS, 15 DIODES

Dimensions: W: 13 1/4"; H: 8 1/2"; D: 11 1/8"

Weight: 17.6 lb

FOR/FOA SYDNEY: TS 500, \$480.00; PS 500 AC, \$96.00

CONSULT YOUR LOCAL RADIO DEALER, OR

MAIL THIS COUPON *today*

Please forward free illustrated literature and specifications on Trio equipment.

Name _____

Address _____



(A unit of Jacoby Mitchell Holdings Ltd.)
376 EASTERN VALLEY WAY, ROSEVILLE, N.S.W.
Cables and Telegraphic Address: "WESTELEC";
Sydney. Phone: 40 1212

LOW DRIFT CRYSTALS



1.6 Mc. to 10 Mc.,
0.005% Tolerance, \$5



10 Mc. to 18 Mc.,
0.005% Tolerance, \$6



Regrinds \$3

THESE PRICES ARE SUBJECT
TO SALES TAX

SPECIAL CRYSTALS:
PRICES
ON APPLICATION

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

Phone 83-5090

LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages
with more writing space.

Price 75c each

plus 17 Cents Post and Wrapping

Obtainable from your Divisional
Secretary, or W.I.A., P.O. Box 36,
East Melbourne, C.2, Victoria.

HY-GAIN (U.S.A.) ANTENNAS AND BEAMS

- 18HT 50 ft. Hy-Tower for 80 through 10 metres.
- 14AVQ 40 through 10 metres, and 18AVQ 80 through 10 metres Trap Verticals.
- 103BA, 153BA, 204BA Mono-band Beams for 10, 15 and 20 metres.
- TH6DXX, TH3MK3, TH3Jr Tri-band Beams.
- 2BDQ and 5BDQ Multi-band Trap Dipoles.
- 18TD Reel Tape Portable Dipole, 10 through 80 metres.
- C.I. Special Plastic Dipole, mil. spec., centre insulator, accepts $\frac{1}{4}$ " or $\frac{3}{8}$ " co-ax.
- E.I. Rugged 7" End Insulators for multi-band or single band dipoles.
- BN-86 all band H.F. Ferrite Baluns for Beams and Dipoles.
- Selection of spare parts for replacement purposes.

ALSO A LARGE RANGE OF V.H.F. ANTENNAS—

6 mx and 2 mx Ground Planes, V.H.F. Mobile Whips, 6 mx and 2 mx Halos. SJ2S4 4-element 2 mx stacked Vertical Jay-Pole. V.H.F. Beams, DB62 Duo-bander for 6 and 2 mx, LP62 Log Periodic for 6 and 2 mx, 215B 15-element 2 mx, 28B 8-element 2 mx, 23B 3-element 2 mx, 66B 6-element 6 mx.

Imported from U.S.A. by HY-GAIN ELECTRONIC PRODUCTS (AUST.) PTY. LTD.

Distributors: **BAIL ELECTRONIC SERVICES**

60 SHANNON STREET, BOX HILL NORTH, VIC., 3129

Phone 89-2213



BIG THINGS in SMALL TRANSFORMERS

Today, with the emphasis on smaller components our own lamination and heat-treatment section can cater for your special needs for small transformers. Consult us also for all small TRIMAX power or audio transformer requirements. The Transformer above is a typical example of a specially developed low-level TRIMAX unit in a Mu-metal case. Overall size is only $1\frac{1}{2}$ " diameter by $1\frac{1}{2}$ " deep.



L M ERICSSON PTY. LTD.

"TRIMAX" DIVISION

FACTORY: CHR. WILLIAMS RD. & CHARLES ST., NORTH COBURG, VICTORIA. PHONE: 32-1223 ... TELEGRAPHIC ADDRESS: "TRIMAX" MELB.



LM41

SIDEBAND ELECTRONICS ENGINEERING

Check my August "A.R." issue advertisement for some of the Clearance Sales Bargains of brand new equipment. There may still be a few units left.

I can now accept orders for the YAESU-MUSEN FT-400 Transceivers, delivery soon, price target around \$600, with sales tax and all charges included. The Transceivers will have my own improvements to prevent blowing out final valves and components. Other Yaesu-Musen models will be announced later on, priced competitively, as to be expected.

Write for my NEWS-SHEETS with the latest information on all types of equipment available or expected, from microphones to beams and rotators.

Some of my current Prices:—

- ★ SWAN SW-500C, \$675.
- ★ GALAXY V. Mk. II., \$500.
- ★ HEATH HA-14 Linear Kit, \$150.
- ★ HEATH HW-32A Kit, \$165.
- ★ WEBSTER Bandspanner with spring mounting, \$55.
- ★ HY-GAIN TH-6-DXX with BN-86 Balun, \$200.
- ★ HY-GAIN TH3JR, \$100.
- ★ NEWTRONICS 4-BTV 10-40 M. Vertical, \$55; same for 10-80 M., \$65.
- ★ German W3DZZ 10-80 M. Dipole, with balun and traps, 100 ft. long, for 75 ohm co-ax feedline, a sensible answer to the G5RV contraptions, \$25.

- ★ HAM-M Rotator with 230v. a.c. control-indicator unit, \$180.
- ★ CETRON 572-B/160TL 150w. Triodes for Linears, \$18.
- ★ Soon expected, EIMAC 3-500Z Triodes, \$38. Also Sockets and Chimneys for these valves.
- ★ MATCHED PAIRS of 6HF5 Valves, so necessary for stability and no TVI, \$10.
- ★ Galaxy V. Mk. II. demonstration set, near-new, under warranty, \$450.
- ★ Used Hallicrafters SX-111 Receiver, \$160.
- ★ Used KW-Viceroy Mk. I. SSB Transmitter, \$200.

—Arie Bles

SIDEBAND ELECTRONICS ENGINEERING, Box 23, Springwood, N.S.W., 2777. Phone Springwood 511-394

DYNAMIC MICROPHONE & STAND

★ LOW PROFILE ★ COMPACT ★ STABLE

SPECIFICATIONS:

Impedance: 50 ohms, 50K ohms
 Frequency Range: 80 to 12 Kc.
 Output: —55 db. (0 db. — 1V./dyne Cm2)
 Switch: D.P.D.T. P. to T.
 Housing: Angle adjustable

ROBUST BASE STATION P.A. MICROPHONE



TYPE 45

ZEPHYR PRODUCTS PTY. LTD.

70 BATESFORD ROAD, CHADSTONE, VIC., 3148

Phone 56-7231

Manufacturers of Radio and Electrical Equipment and Components



W.A.— S.A.— Tas.— N.S.W.— Old.—
 Agents: D. K. Northover & Co.; Neil Muller Ltd.; Homecrafts (Tas.) P/L; Jacoby, Mitchell & Co. P/L; T. H. Martin P/L

A LARGE RANGE OF TRANSMITTERS, RECEIVERS, TEST GEAR, AND DISPOSALS RADIO PARTS AVAILABLE

● CRYSTAL CALIBRATOR No. 10

Nominal Frequency Range: 550 Kc. to 30 Mc.
Internal 500 Kc. crystal. VFO frequency coverage: 250-500 Kc. 2 Kc. dial divisions.

Used (good condition): **\$10.50.**

New (sealed cartons): **\$13.00.**

Packing and freight: **\$1.50.**

● TRANSISTORS

2SC73

2SD65

2T65

2T76

OC66

All at Bargain Price of **25 cents each.**

● MILLER 8903B PRE-WIRED I.F. STRIPS

455 Kc. centre frequency, 55 db. gain. Employs two PNP transistors and diode detector.

Price **\$9.50.**

● EICO 753 TRI-BAND S.S.B. TRANSCEIVER

Full CW-AM-SSB coverage, 80-40-20 metres.
180w. PEP SSB-CW. VOX-PTT-ALC. 10 Kc. Receiver offset tuning.

Kit **\$328.78**, Wired **\$428.78.**

● STAR SR700 SSB AMATEUR BAND RECEIVER

Frequency coverage: 3.4-29.7 Mc. in 7 bands. Triple conversion, employs xtal locked 1st and 3rd conversion oscillators. Selectable USB or LSB. Selectivity variable, 0.5 Kc. to 4 Kc. 1 Kc. dial calibration. Three stages double locked geared dial mechanism, 30 Kc. per turn tuning rate. Vackar oscillator employed in VFO for maximum stability.

Price **\$461.50.**

● A111 9 Mc. SSB EXCITER

A fibre-glass printed circuit board, the finest German crystal filter, diode ring modulator, and solid state circuitry all contribute to make the A111 the finest SSB Exciter available. Specifications: Sideband suppression, 80 db.; carrier sup., 65 db.; audio freq. response, 350 to 3,000 cycles; mic. input, 1 mV. on 5K ohm load. Incorporates VOX amplifier and relay amplifier.

Price with KVG XF9B Filter, **\$120.**

● VALVE SPECIALS

807—70 cents ea.

815—70 cents ea.

6AC7—20 cents ea. or 12 for \$2.

6J6—30 cents ea. or 7 for \$2.

6CQ6—20 cents ea. or 6 for \$1.

VR150/30—75 cents ea. or 3 for \$2.

VR105/30—75 cents ea. or 3 for \$2.

QB2/250 (813)—\$7 ea.

TZ40—75 cents ea.

6H6 (Metal)—20 cents ea.

DM71 (Indicator Tube)—40c ea. or 6 for \$2.

● A112 5 Mc. VFO

Frequency coverage: 4950 to 5550 Kc. Frequency stability better than 100 c/s. over 12 hours long term; better than 8 c/s. over 10 minutes if enclosed in suitable box. Output: 350 mV. on 220 ohm load.

Price **\$22.**

WANTED TO BUY

Communication Receivers, Test Equipment, etc. Call, write or phone. Equipment inspected and picked up at your convenience any night or week-end.


ALL ITEMS FREIGHT EXTRA

UNITED TRADE SALES PTY. LTD.

280 LONSDALE ST., MELBOURNE, VIC. (Opp. Myers)

Phone 32-3815

DEPENDENT ON P^E CRYSTALS

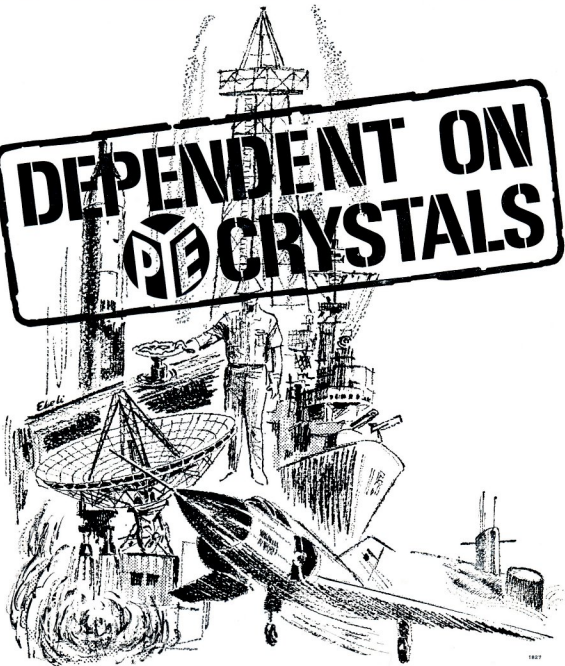

PYE PTY.
LTD.

Q.C.B. APPROVED ORGANISATION



P.O. BOX 105, CLAYTON, VICTORIA, 3168

Tel. 544-0361

Telegrams: "PYTRONIC" MELBOURNE

Brisbane, Sydney, Adelaide, Perth, Hobart, Canberra, Geelong.